



Favio Andrés Acosta David

COMPONENTS LIBRARY

PUBLISHED BY UNIVERSIDAD DE LOS ANDES - COLOMBIA



This work is licensed under a Creative Commons Attribution-NonCommercial-NoDerivatives 4.0 International License.

December 2020 - Bogotá D.C.

Contents

1	Universal Asynchronous Receiver Transmitter (UART).	5
1.1	Transmitter (TX)	5
1.1.1	Component description	5
1.1.2	Symbol	6
1.1.3	Port description	6
1.1.4	Black box diagram	7
1.1.5	Functionality	7
1.1.6	Reference model	9
1.1.7	HDL: Black box	11
1.1.8	Test vector definition	12
1.1.9	HDL: Test vectors	13
1.1.10	White box diagram	15
1.1.11	HDL: White box	16
1.1.12	HDL: Blocks	19
1.1.13	Temporal simulation	19
1.1.14	Resource utilization	20
1.1.15	Quartus diagrams	20
1.1.16	Physical implementation	21
1.1.17	Results and learnt lessons	23
1.2	Receptor (RX)	24
1.2.1	Component description	24
1.2.2	Symbol	24
1.2.3	Port description	25
1.2.4	Black box diagram	25
1.2.5	Functionality	26
1.2.6	Reference model	28
1.2.7	HDL: Black box	30
1.2.8	Test vector definition	31
1.2.9	HDL: Test vectors	31
1.2.10	White box diagram	33



1.2.11	HDL: White box	34
1.2.12	HDL: Blocks	36
1.2.13	Temporal simulation	36
1.2.14	Resource utilization	37
1.2.15	Quartus diagrams	38
1.2.16	Physical implementation	38
1.2.17	Results and learnt lessons	39

2 Serial Peripheral Interface (SPI). 41

2.1 Master (M) 41

2.1.1	Component description	41
2.1.2	Symbol	42
2.1.3	Port description	42
2.1.4	Black box diagram	43
2.1.5	Functionality	44
2.1.6	Reference model	46
2.1.7	HDL: Black box	49
2.1.8	Test vector definition	50
2.1.9	HDL: Test vectors	50
2.1.10	White box diagram	53
2.1.11	HDL: White box	53
2.1.12	HDL: Blocks	57
2.1.13	Temporal simulation	57
2.1.14	Resource utilization	58
2.1.15	Quartus diagrams	58
2.1.16	Physical implementation	59
2.1.17	Results and learnt lessons	61

2.2 Slave (S) 62

2.2.1	Component description	62
2.2.2	Symbol	62
2.2.3	Port description	63
2.2.4	Black box diagram	63
2.2.5	Functionality	64
2.2.6	Reference model	66
2.2.7	HDL: Black box	68
2.2.8	Test vector definition	69
2.2.9	HDL: Test vectors	70
2.2.10	White box diagram	72
2.2.11	HDL: White box	72
2.2.12	HDL: Blocks	75
2.2.13	Temporal simulation	75
2.2.14	Resource utilization	76
2.2.15	Quartus diagrams	77
2.2.16	Physical implementation	77
2.2.17	Results and learnt lessons	80

1. Universal Asynchronous Receiver Transmitter (UART).

Favio Acosta

In some way, asynchronous serial communication between devices, is analogous to human communication. Both don't require to be precise, just to be understandable.

Components designed:

Along this chapter, the asynchronous serial communication protocol UART will be exposed, showing the transmitter (TX) block and the receptor block (RX) with its specific features governed by the protocol definition.

1.1 Transmitter (TX)

Below, the serial communication component **UART Transmitter (TX)** is presented, showing its protocol to send information. To consult the whole UART transmitter core and its source codes, the next repository link can be followed: https://github.com/favioacostad/UART_IP_Core/tree/main/PJRO_UART_TX

1.1.1 Component description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student understands and proposes product specifications and restrictions.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate, and consistent) that explain: constraints, specifications, and search and identification of contexts where that component is used.

- The description of the component is written in the student words, organized logically and clearly.
- The specifications and restrictions fully respond to the requested component, demonstrating originality and own contributions.
- The search and identification of contexts where this component is used is clear.
- Discipline language is accurate and appropriate, phrases are grammatically correct and there are no spelling errors.

The serial transmitter port for UART is a module widely used into the System on Chip (SoC) communication field to transmit information between devices. It is asynchronous, which means that is necessary to establish a baud (Bits/Sec) rate as an agreement of both terminals. Regarding the data frame sent by **tx**, it has a one logic value (high level), until the input **newData** points



out, with another logic value of one, that there's a new byte to transmit. With this intention, the **tx** output starts to send the data frame to its destiny.


It is important to realize the restrictions in terms of data transfer speed, measured in bauds. In general, there's some limited special values devices support, which bounds are 4800 and 256000 bauds. A value up to this range, although is possible with the protocol designed, is rarely used. Another key point to highlight are the voltage values that represent the high and low logic levels; in the case of *DE0-Nano* where this component was developed, the values are **3.3V** and **0V** respectively.

1.1.2 Symbol

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates his component to a generic symbol usable in an architectural diagram.
DELIVERABLES: Correct and complete diagram.

 - The symbol proposed to represent the component is based on symbols of a similar nature presented in the electronic component literature.



1.1.3 Port description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student recognizes all the Input/Output (I/O) ports the module has.
DELIVERABLES: A description of each I/O port signal where its type, size and initial state are enunciated.

- The whole I/O signal ports are explicitly described and it is easy to understand the functionality for each one into the core.
- It is clear for the input ports, what kind of signal has to be stimulated to get a correct performance.



I/O Ports description				
Name	Signal type	Size	Initial state	Description
BB_SYSTEM_tx_Out	Output	1	1	Transmitter signal in charge of carrying the data based on the baud rate.
BB_SYSTEM_busy_Out	Output	1	0	Boolean signal to indicate if the module is currently busy or idle.
BB_SYSTEM_CLOCK_50	Input	1	-	Clock of the system with a default value of 50MHz.
BB_SYSTEM_RESET_InHigh	Input	1	0	Reset signal in case of reload the initial values for the module.
BB_SYSTEM_LOCK_InHigh	Input	1	0	Boolean signal to lock or not the module from an external signal.
BB_SYSTEM_newData_InHigh	Input	1	0	Boolean signal to inform of new data from an external module.
BB_SYSTEM_data_In	Input	8	00000000	Data in terms of bytes to transmit.


1.1.4 Black box diagram

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies input/output signals for the product.

DELIVERABLES: Correct and complete diagram.

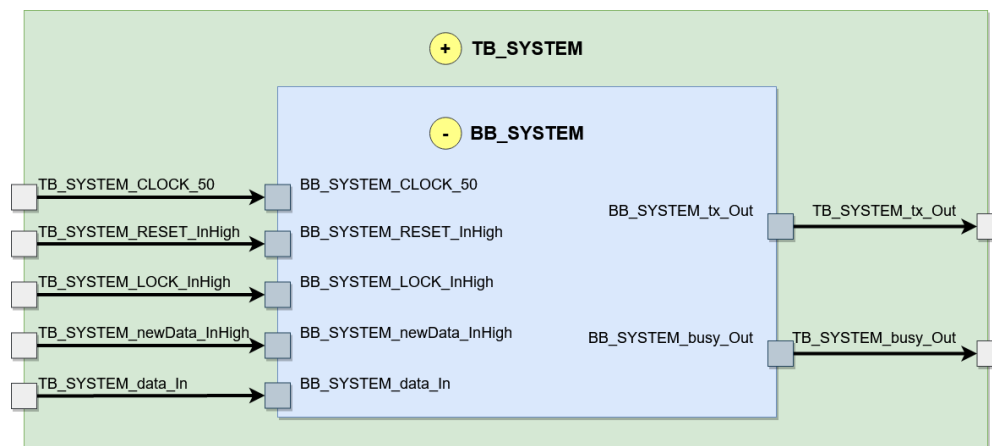- There is full correspondence between the black box diagram and the functionality of the requested component.
- The black box diagram shows all input and output signals with their corresponding structured names (In/Out) and sizes (bit/bus).
- The black box diagram relates that component to the characterization diagram (test-bench).



1.1.5 Functionality

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student breaks down the problem into a set of steps that respond to the expected functionality.

DELIVERABLES: Equation / Truth Table / Macro-algorithm correct and complete according to component functionality.

- The character equation and/or truth table and/or solution macro-algorithm correctly describes the functionality of the component and is properly represented by a detailed explanation where each step is less complex than the requested component.



Characteristic equation

$$data_In[7:0] \leq (data_In[7], data_In[6], \dots, data_In[0])_{CLOCK_PER_BIT} \leq tx_Out$$



Truth table

INPUTS			OUTPUTS	
RESET_In	LOCK_In	newData_In	tx_Out	busy_Out
0	0	0	1	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0



Macro-algorithm

Algorithm 1: Transmitter port TX

Data:

RESET_In, LOCK_In, newData_In, [7:0] data_In

Algorithm:

tx_Out = 1

busy_Out = 0

counter = 0

counterBit = 0

CLOCK_PER_BIT = Freq/BaudRate

if not RESET_In:

case state:

LOCKED_IDLE:

if LOCK_In:

busy_Out = 1

else:

state = UNLOCKED_IDLE

UNLOCKED_IDLE:

if newData_In:

busy_Out = 0

state = START_BIT

START_BIT:

tx_Out = 0

busy_Out = 1

counter += 1

if counter == CLOCK_PER_BIT:

counter = 0

state = DATA_INIT

**Algorithm 2:** Transmitter port TX

```

DATA_INIT:
    counter += 1
    if counter == CLOCK_PER_BIT:
        counter = 0
        state = DATA_END

DATA_END:
    tx_Out = data_In[counterBit]
    counterBit += 1
    if counterBit == 7:
        counterBit = 0
        counter = 0
        state = STOP_BIT
    else:
        state = DATA_INIT

STOP_BIT:
    tx_Out = 1
    busy_Out = 1
    counter += 1
    if counter == CLOCK_PER_BIT:
        counter = 0
        state = LOCKED_IDLE
end case

```

Results:

tx_Out, busy_Out

1.1.6 Reference model**QUALITY PRODUCT:**

PEDAGOGICAL OBJECTIVE: The student proposes a reference model as function verification and control verification of RTL models, which can be constructed with software high level languages like C, C++, JavaScript, Python, etc.

DELIVERABLES: Source codes.

- The description in software language has similar structure to the hardware language algorithm.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.
- The validation model verifies the consistency of the RTL modules by judging whether the two designs are equivalent and consistent.

The source code below, just depicts the function based on the UART White Box module for transmission. To consult the whole reference model, it is necessary to visit the next on-line repository: https://github.com/favioacostad/UART_IP_Core/tree/main/PJR0_UART_TX/reference.

```

1 #=====
2 # LIBRARIES Definition
3 #=====
4 # Libraries required along the code
5 import numpy as np
6 np.set_printoptions(threshold = np.inf)
7
8 #=====
9 # MODULE Definition
10 #=====
11 # Function describing UART serial communication protocol for transmission
12 def UART_TX (UART_TX_CLOCK_S0, UART_TX_RESET_InHigh, UART_TX_LOCK_InHigh, UART_TX_newData_InHigh, UART_TX_data_In ,
13             CLOCK_PER_BIT, DATAWIDTH_BUS, STATE_SIZE):
14
15 #=====
16 # PARAMETER Declarations

```



```
17 #=====
18 #////////// STATES //////////
19 State_LOCKED_IDLE = np.uint8(0)
20 State_UNLOCKED_IDLE = np.uint8(1)
21 State_START_BIT = np.uint8(2)
22 State_DATA_INIT = np.uint8(3)
23 State_DATA_END = np.uint8(4)
24 State_STOP_BIT = np.uint8(5)
25 #////////// SIZES //////////
26 # Ceiling of log base 2 to get the number of bits needed to store a value
27 # CLOCK_PER_BIT = 50MHz/256000Bauds
28 COUNTER_SIZE = int(np.log2(CLOCK_PER_BIT)) # 8 bits

30 #=====
31 # PORT Declarations
32 #=====
33 #////////// OUTPUTS //////////
34 # Default values
35 UART_TX_tx_Out = np.uint8(1)
36 UART_TX_busy_Out = np.uint8(0)

38 #=====
39 # REG/WIRE Declarations
40 #=====
41 # Registers (Q)
42 global Tx_Register, Busy_Register, State_Register, Lock_Register
43 global NewData_Register, Data_Register, Counter_Register, BitCounter_Register

45 #=====
46 # STRUCTURAL Coding
47 #=====
48 # INPUT LOGIC: Combinational
49 # Signals (D)
50 Lock_Signal = UART_TX_LOCK_InHigh
51 NewData_Signal = UART_TX_newData_InHigh
52 Data_Signal = Data_Register
53 State_Signal = State_Register
54 Counter_Signal = Counter_Register
55 BitCounter_Signal = BitCounter_Register

57 if State_Register == State_LOCKED_IDLE:
58     if Lock_Register:
59         State_Signal = State_LOCKED_IDLE
60     else:
61         State_Signal = State_UNLOCKED_IDLE

63 elif State_Register == State_UNLOCKED_IDLE:
64     Counter_Signal = 0
65     BitCounter_Signal = 0
66     if NewData_Register:
67         State_Signal = State_START_BIT
68         Data_Signal = UART_TX_data_In
69     elif not NewData_Register and not Lock_Register:
70         State_Signal = State_UNLOCKED_IDLE
71     else:
72         State_Signal = State_LOCKED_IDLE

74 elif State_Register == State_START_BIT:
75     Counter_Signal = Counter_Register + 1
76     if Counter_Register == CLOCK_PER_BIT-1:
77         State_Signal = State_DATA_INIT
78         Counter_Signal = 0
79     else:
80         State_Signal = State_START_BIT

82 elif State_Register == State_DATA_INIT:
83     Counter_Signal = Counter_Register + 1
84     if Counter_Register == CLOCK_PER_BIT-1:
85         State_Signal = State_DATA_END
86         Counter_Signal = 0
87     else:
88         State_Signal = State_DATA_INIT

90 elif State_Register == State_DATA_END:
91     BitCounter_Signal = BitCounter_Register + 1
92     if BitCounter_Register == DATAWIDTH_BUS-1:
93         State_Signal = State_STOP_BIT
94         Counter_Signal = 0
95     else:
96         State_Signal = State_DATA_INIT

98 elif State_Register == State_STOP_BIT:
99     Counter_Signal = Counter_Register + 1
100     if Counter_Register == CLOCK_PER_BIT-1:
101         State_Signal = State_LOCKED_IDLE
102         Counter_Signal = 0
103     else:
104         State_Signal = State_STOP_BIT

106 else:
107     State_Signal = State_LOCKED_IDLE

109 #=====
110 # OUTPUTS
111 #=====
```



```
112 # OUTPUT LOGIC: Combinational
113 # Signals (D)
114 Tx_Signal = Tx_Register
115 Busy_Signal = Busy_Register

117 if State_Register == State_LOCKED_IDLE:
118     Tx_Signal = np.uint8(1)
119     Busy_Signal = np.uint8(1)

121 elif State_Register == State_UNLOCKED_IDLE:
122     Tx_Signal = np.uint8(1)
123     Busy_Signal = np.uint8(0)

125 elif State_Register == State_START_BIT:
126     Tx_Signal = np.uint8(0)
127     Busy_Signal = np.uint8(1)

129 elif State_Register == State_DATA_INIT:
130     Tx_Signal = Data_Register[BitCounter_Register]
131     Busy_Signal = np.uint8(1)

133 elif State_Register == State_DATA_END:
134     Tx_Signal = Data_Register[BitCounter_Register]
135     Busy_Signal = np.uint8(1)

137 elif State_Register == State_STOP_BIT:
138     Tx_Signal = np.uint8(1)
139     Busy_Signal = np.uint8(1)

141 else:
142     Tx_Signal = np.uint8(1)
143     Busy_Signal = np.uint8(0)

145 # STATE REGISTER : Sequential
146 if UART_TX_CLOCK_50:
147     # Updating global registers
148     if UART_TX_RESET_InHigh:
149         Tx_Register = np.uint8(1)
150         Busy_Register = np.uint8(0)
151         State_Register = State_LOCKED_IDLE
152         Lock_Register = np.uint8(0)
153         NewData_Register = np.uint8(0)
154         Data_Register = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
155         Counter_Register = 0
156         BitCounter_Register = 0
157     else:
158         Tx_Register = Tx_Signal
159         Busy_Register = Busy_Signal
160         State_Register = State_Signal
161         Lock_Register = Lock_Signal
162         NewData_Register = NewData_Signal
163         Data_Register = Data_Signal
164         Counter_Register = Counter_Signal
165         BitCounter_Register = BitCounter_Signal

167 # OUTPUT ASSIGNMENTS
168 UART_TX_tx_Out = Tx_Register
169 UART_TX_busy_Out = Busy_Register

171 return UART_TX_tx_Out, UART_TX_busy_Out
```

Archive 1.1: REF_SYSTEM.py

1.1.7 HDL: Black box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```
1 /> #####
2 /** G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3 #####
4 /** Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5 /** Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6 /**
7 /** This program is free software: you can redistribute it and/or modify
8 /** it under the terms of the GNU General Public License as published by
9 /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
```



```

14  ## GNU General Public License for more details.
15  ##
16  ## You should have received a copy of the GNU General Public License
17 ## along with this program. If not, see <http://www.gnu.org/licenses/>
18 ##### s/
19
20 =====
21 // MODULE Definition
22 =====
23 module BB_SYSTEM (
24 ////////// OUTPUTS //////////
25     BB_SYSTEM_tx_Out ,
26     BB_SYSTEM_busy_Out ,
27 ////////// INPUTS //////////
28     BB_SYSTEM_CLOCK_50 ,
29     BB_SYSTEM_RESET_InHigh ,
30     BB_SYSTEM_LOCK_InHigh ,
31     BB_SYSTEM_newData_InHigh ,
32     BB_SYSTEM_data_In
33 );
34
35 =====
36 // PARAMETER Declarations
37 =====
38 ////////// BAUD RATE //////////
39 // Ratio between the internal frequency and the baud rate
40 parameter CLOCK_PER_BIT = 434; // CLOCK_PER_BIT = 50MHz/115200 Bauds
41 // parameter CLOCK_PER_BIT = 868; // CLOCK_PER_BIT = 50MHz/57600 Bauds
42 // parameter CLOCK_PER_BIT = 2604; // CLOCK_PER_BIT = 50MHz/19200 Bauds
43 // parameter CLOCK_PER_BIT = 5208; // CLOCK_PER_BIT = 50MHz/9600 Bauds
44 ////////// SIZES //////////
45 // Data width of the input bus
46 parameter DATAWIDTH_BUS = 8;
47 // Size for the states needed into the protocol
48 parameter STATE_SIZE = 3;
49
50 =====
51 // PORT Declarations
52 =====
53 ////////// OUTPUTS //////////
54 output BB_SYSTEM_tx_Out;
55 output BB_SYSTEM_busy_Out;
56 ////////// INPUTS //////////
57 input BB_SYSTEM_CLOCK_50;
58 input BB_SYSTEM_RESET_InHigh;
59 input BB_SYSTEM_LOCK_InHigh;
60 input BB_SYSTEM_newData_InHigh;
61 input [DATAWIDTH_BUS-1:0] BB_SYSTEM_data_In;
62
63 =====
64 // REG/WIRE Declarations
65 =====
66
67 =====
68 // STRUCTURAL Coding
69 =====
70 UART_TX #(CLOCK_PER_BIT(CLOCK_PER_BIT), .DATAWIDTH_BUS(DATAWIDTH_BUS), .STATE_SIZE(STATE_SIZE)) UART_TX_u0 (
71 // Port map - connection between master ports and signals/registers
72 ////////// OUTPUTS //////////
73     .UART_TX_tx_Out(BB_SYSTEM_tx_Out) ,
74     .UART_TX_busy_Out(BB_SYSTEM_busy_Out) ,
75 ////////// INPUTS //////////
76     .UART_TX_CLOCK_50(BB_SYSTEM_CLOCK_50) ,
77     .UART_TX_RESET_InHigh(BB_SYSTEM_RESET_InHigh) ,
78     .UART_TX_LOCK_InHigh(BB_SYSTEM_LOCK_InHigh) ,
79     .UART_TX_newData_InHigh(BB_SYSTEM_newData_InHigh) ,
80     .UART_TX_data_In(BB_SYSTEM_data_In)
81 );
82
83 endmodule

```

Archive 1.2: BB_SYSTEM.v

1.1.8 Test vector definition

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student proposes a strategy to validate the functionality of the product.

DELIVERABLES: Clear selection strategies. Clear explanation of operation.

- Test vectors are selected by describing an explicit and clearly defined strategy in a paragraph, and these vectors allow you to fully verify functionality.

The test vectors are composed first, by the reset input; second, by the lock input, which allows to lock the module of receiving any information; and third, there's the new data input that informs about information to send available at the fourth, the input data in. The subsequent values are set to this data input which has the size of a byte (8 bits); these values are related



with the ASCII (American Standard Code for Information Interchange) table and coincide to the characters: '0', '1', '2', '3', ..., '9'; 'a', 'b', 'c', ..., 'j'.

TEST VECTOR INPUTS			
RESET_In	LOCK_In	newData_In	data_In
1	1	0	00000000
0	1	0	00000000
0	0	0	00000000
0	0	1	00000000
0	0	1	00110000
0	0	1	00110001
0	0	1	00110010
0	0	1	00110011
0	0	1	...
0	0	1	00111001
0	0	1	01100001
0	0	1	01100010
0	0	1	...
0	0	1	01101010
0	0	0	00000000
0	0	0	00000001

1.1.9 HDL: Test vectors

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.


DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* *****
2  /** G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  /** *****
4  /** Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /** Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /**
7  /** This program is free software: you can redistribute it and/or modify
8  /** it under the terms of the GNU General Public License as published by
9  /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /** GNU General Public License for more details.
15 /**
16 /** You should have received a copy of the GNU General Public License
17 /** along with this program. If not, see <http://www.gnu.org/licenses/>
18 /** ***** */
19
20 /** =====
21 /** MODULE Definition
22 /** =====
23 /** Escala de tiempo
24 /** timescale 1 ns / 1 ns
25 module TB_SYSTEM();
26 /** Constants
27 /** =====
28 /** Parameter (May differ for physical synthesis)
29 /** =====
30 /** General purpose registers
31 reg eachvec;
32 parameter TCK = 20; // Clock period in ns
33 parameter CLK_FREQ = 1000000000 / TCK; // Frequency in HZ
34 parameter DATAWIDTH_BUS = 8;
35 parameter CLOCK_PER_BIT = 434; // CLOCK_PER_BIT = 50MHz/115200Bauds
36 // parameter CLOCK_PER_BIT = 868; // CLOCK_PER_BIT = 50MHz/57600Bauds
37 // parameter CLOCK_PER_BIT = 2604; // CLOCK_PER_BIT = 50MHz/19200Bauds

```

 





```
111 TB_SYSTEM_newData_InHigh <= 1'b1; TB_SYSTEM_data_In <= 8'b01101001;
    #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b0;
    TB_SYSTEM_newData_InHigh <= 1'b1; TB_SYSTEM_data_In <= 8'b01101010;
112
113 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b0;
    TB_SYSTEM_newData_InHigh <= 1'b0; TB_SYSTEM_data_In <= 8'b00000000;
114 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b0;
    TB_SYSTEM_newData_InHigh <= 1'b0; TB_SYSTEM_data_In <= 8'b00000000;
115 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b0;
    TB_SYSTEM_newData_InHigh <= 1'b0; TB_SYSTEM_data_In <= 8'b00000000;
116 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b0;
    TB_SYSTEM_newData_InHigh <= 1'b0; TB_SYSTEM_data_In <= 8'b00000000;
117
118 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b1;
    TB_SYSTEM_newData_InHigh <= 1'b0; TB_SYSTEM_data_In <= 8'b00000001;
119 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b1;
    TB_SYSTEM_newData_InHigh <= 1'b0; TB_SYSTEM_data_In <= 8'b00000010;
120 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b1;
    TB_SYSTEM_newData_InHigh <= 1'b1; TB_SYSTEM_data_In <= 8'b00000011;
121 #(TCK*(DATAWIDTH_BUS+2)*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_LOCK_InHigh <= 1'b1;
    TB_SYSTEM_newData_InHigh <= 1'b1; TB_SYSTEM_data_In <= 8'b00000100;
122
123 // #(TCK*10000) $finish;
124 @eachvec;
125 $finish;
126 // --> end
127 end
128 endmodule
```

Archive 1.3: TB_SYSTEM.vt

1.1.10 White box diagram


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student makes a diagram of sub-components, signals and interconnections and makes a description of each sub-component.

DELIVERABLES: Diagram of sub-components, signals and interconnections, description of component or component to component.

- The white box diagram is correct and corresponds to the requested component.
- All internal and input/output signals with their corresponding structured names (In/Out) and sizes (Bit/Bus) are displayed for all internal system components.
- The white box diagram corresponds to an efficient solution in terms of resources, number of blocks and elements and solution algorithm. Internal components are less complex than those with higher hierarchy.
- A description (what is and how it works) of each of the constituent components of the requested component is presented, describing its signals.

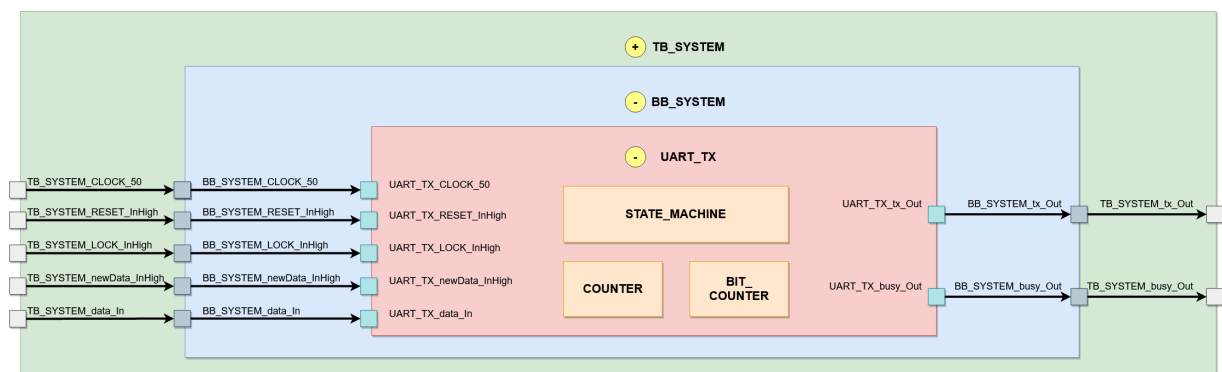For this specific case, the input/output ports match with the higher module into the hierarchical design.





1.1.11 HDL: White box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* #####
2  /** G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  #####
4  /** Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /** Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /**
7  /** This program is free software: you can redistribute it and/or modify
8  /** it under the terms of the GNU General Public License as published by
9  /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /** GNU General Public License for more details.
15 /**
16 /** You should have received a copy of the GNU General Public License
17 /** along with this program. If not, see <http://www.gnu.org/licenses/>
18 /** ##### */

20 //=====
21 // MODULE Definition
22 //=====
23 module UART_TX #(parameter CLOCK_PER_BIT, parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 /////////////// OUTPUTS ///////////////////
25     UART_TX_tx_Out,
26     UART_TX_busy_Out,
27 /////////////// INPUTS ///////////////////
28     UART_TX_CLOCK_50,
29     UART_TX_RESET_InHigh,
30     UART_TX_LOCK_InHigh,
31     UART_TX_newData_InHigh,
32     UART_TX_data_In
33 );

35 //=====
36 // PARAMETER Declarations
37 //=====
38 /////////////// STATES ///////////////////
39 localparam State_LOCKED_IDLE = 3'b000;
40 localparam State_UNLOCKED_IDLE = 3'b001;
41 localparam State_START_BIT = 3'b010;
42 localparam State_DATA_INIT = 3'b011;
43 localparam State_DATA_END = 3'b100;
44 localparam State_STOP_BIT = 3'b101;
45 /////////////// SIZES ///////////////////
46 // Ceiling of log base 2 to get the number of bits needed to store a value
47 // CLOCK_PER_BIT = 50MHz/115200Bauds
48 localparam COUNTER_SIZE = $clog2(CLOCK_PER_BIT); // 8 bits

50 //=====
51 // PORT Declarations
52 //=====
53 /////////////// OUTPUTS ///////////////////
54 output UART_TX_tx_Out;
55 output UART_TX_busy_Out;
56 /////////////// INPUTS ///////////////////
57 input UART_TX_CLOCK_50;
58 input UART_TX_RESET_InHigh;
59 input UART_TX_LOCK_InHigh;
60 input UART_TX_newData_InHigh;
61 input [DATAWIDTH_BUS-1:0] UART_TX_data_In;
62 /////////////// FLAGS ///////////////////

64 //=====
65 // REG/WIRE Declarations
66 //=====
67 /////////////// REGISTERS ///////////////////
68 // Transmitter
69 reg Tx_Register;
70 // Boolean variable to indicate if the module is currently busy or idle
71 reg Busy_Register;
72 // Current state of the protocol
73 reg [STATE_SIZE-1:0] State_Register;
74 // Boolean variable to lock or not the module
75 reg Lock_Register;
76 // Boolean variable to inform of new data
77 reg NewData_Register;
78 // Data in terms of bytes
79 reg [DATAWIDTH_BUS-1:0] Data_Register;
80 // Counter for the clock cycles carried out so far

```



```
81 reg [COUNTER_SIZE-1:0] Counter_Register;
82 // Counter for the number of bits carried out so far
83 reg [2:0] BitCounter_Register;
84 ////////////// SIGNALS //////////////////
85 reg Tx_Signal;
86 reg Busy_Signal;
87 reg [STATE_SIZE-1:0] State_Signal;
88 reg Lock_Signal;
89 reg NewData_Signal;
90 reg [DATAWIDTH_BUS-1:0] Data_Signal;
91 reg [COUNTER_SIZE-1:0] Counter_Signal;
92 reg [2:0] BitCounter_Signal;

94 //=====
95 // STRUCTURAL Coding
96 //=====
97 // INPUT LOGIC: Combinational
98 always @(*)
99 begin
100 // To init registers
101 // State_Signal = State_Register;
102 Lock_Signal = UART_TX_LOCK_InHigh;
103 NewData_Signal = UART_TX_newData_InHigh;
104 Data_Signal = Data_Register;
105 Counter_Signal = Counter_Register;
106 BitCounter_Signal = BitCounter_Register;
107
108 case (State_Register)
109   State_LOCKED_IDLE:
110     begin
111       if (Lock_Register)
112         State_Signal = State_LOCKED_IDLE;
113       else
114         State_Signal = State_UNLOCKED_IDLE;
115     end
116
117   State_UNLOCKED_IDLE:
118     begin
119       Counter_Signal = {COUNTER_SIZE{1'b0}};
120       BitCounter_Signal = 3'b000;
121       if (NewData_Register)
122         begin
123           State_Signal = State_START_BIT;
124           Data_Signal = UART_TX_data_In;
125         end
126       else if (~NewData_Register & ~Lock_Register)
127         State_Signal = State_UNLOCKED_IDLE;
128       else
129         State_Signal = State_LOCKED_IDLE;
130     end
131
132   State_START_BIT:
133     begin
134       Counter_Signal = Counter_Register + 1'b1;
135       if (Counter_Register == CLOCK_PER_BIT-1)
136         begin
137           State_Signal = State_DATA_INIT;
138           Counter_Signal = {COUNTER_SIZE{1'b0}};
139         end
140       else
141         State_Signal = State_START_BIT;
142     end
143
144   State_DATA_INIT:
145     begin
146       Counter_Signal = Counter_Register + 1'b1;
147       if (Counter_Register == CLOCK_PER_BIT-1)
148         begin
149           State_Signal = State_DATA_END;
150           Counter_Signal = {COUNTER_SIZE{1'b0}};
151         end
152       else
153         State_Signal = State_DATA_INIT;
154     end
155
156   State_DATA_END:
157     begin
158       BitCounter_Signal = BitCounter_Register + 1'b1;
159       if (BitCounter_Register == DATAWIDTH_BUS-1)
160         begin
161           State_Signal = State_STOP_BIT;
162           Counter_Signal = {COUNTER_SIZE{1'b0}};
163           BitCounter_Signal = 3'b000;
164         end
165       else
166         State_Signal = State_DATA_INIT;
167     end
168
169   State_STOP_BIT:
170     begin
171       Counter_Signal = Counter_Register + 1'b1;
172       if (Counter_Register == CLOCK_PER_BIT-1)
173         begin
174           State_Signal = State_LOCKED_IDLE;
175           Counter_Signal = {COUNTER_SIZE{1'b0}};
```



```
176         end
177     else
178         State_Signal = State_STOP_BIT;
179     end
180
181     default: State_Signal = State_LOCKED_IDLE;
182 endcase
183 end
184
185 // STATE REGISTER : Sequential
186 always @(posedge UART_TX_CLOCK_50, posedge UART_TX_RESET_InHigh)
187 begin
188     if (UART_TX_RESET_InHigh)
189     begin
190         Tx_Register <= 1'b1;
191         Busy_Register <= 1'b0;
192         State_Register <= State_LOCKED_IDLE;
193         Lock_Register <= 1'b0;
194         NewData_Register <= 1'b0;
195         Data_Register <= {DATAWIDTH_BUS{1'b0}};
196         Counter_Register <= {COUNTER_SIZE{1'b0}};
197         BitCounter_Register <= 3'b000;
198     end
199
200     else
201     begin
202         Tx_Register <= Tx_Signal;
203         Busy_Register <= Busy_Signal;
204         State_Register <= State_Signal;
205         Lock_Register <= Lock_Signal;
206         NewData_Register <= NewData_Signal;
207         Data_Register <= Data_Signal;
208         Counter_Register <= Counter_Signal;
209         BitCounter_Register <= BitCounter_Signal;
210     end
211 end
212
213 // =====
214 // OUTPUTS
215 // =====
216 // OUTPUT LOGIC: Combinational
217 always @(*)
218 begin
219     // To init registers
220     // Busy_Signal = Busy_Register;
221     // Tx_Signal = Tx_Register;
222
223     case (State_Register)
224     State_LOCKED_IDLE:
225     begin
226         Tx_Signal = 1'b1;
227         Busy_Signal = 1'b1;
228     end
229
230     State_UNLOCKED_IDLE:
231     begin
232         Tx_Signal = 1'b1;
233         Busy_Signal = 1'b0;
234     end
235
236     State_START_BIT:
237     begin
238         Tx_Signal = 1'b0;
239         Busy_Signal = 1'b1;
240     end
241
242     State_DATA_INIT:
243     begin
244         Tx_Signal = Data_Register[BitCounter_Register];
245         Busy_Signal = 1'b1;
246     end
247
248     State_DATA_END:
249     begin
250         Tx_Signal = Data_Register[BitCounter_Register];
251         Busy_Signal = 1'b1;
252     end
253
254     State_STOP_BIT:
255     begin
256         Tx_Signal = 1'b1;
257         Busy_Signal = 1'b0;
258     end
259
260     default:
261     begin
262         Tx_Signal = 1'b1;
263         Busy_Signal = 1'b0;
264     end
265 endcase
266 end
267
268 // OUTPUT ASSIGNMENTS
269 assign UART_TX_tx_Out = Tx_Register;
270 assign UART_TX_busy_Out = Busy_Register;
```

272 `endmodule`

Archive 1.4: WB_SYSTEM.v

1.1.12 HDL: Blocks

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

From this particular case, there's no elements of lower hierarchy.

1.1.13 Temporal simulation


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates the functionality according to the proposed specifications with various types of tests.


DELIVERABLES: Functionality according to the proposed specifications and in various types of tests.

- Simulation results are presented for the requested product, explaining three or more operating cases on the simulation diagram. The simulation contains markers on the graph that indicate specific situations of the prototype.

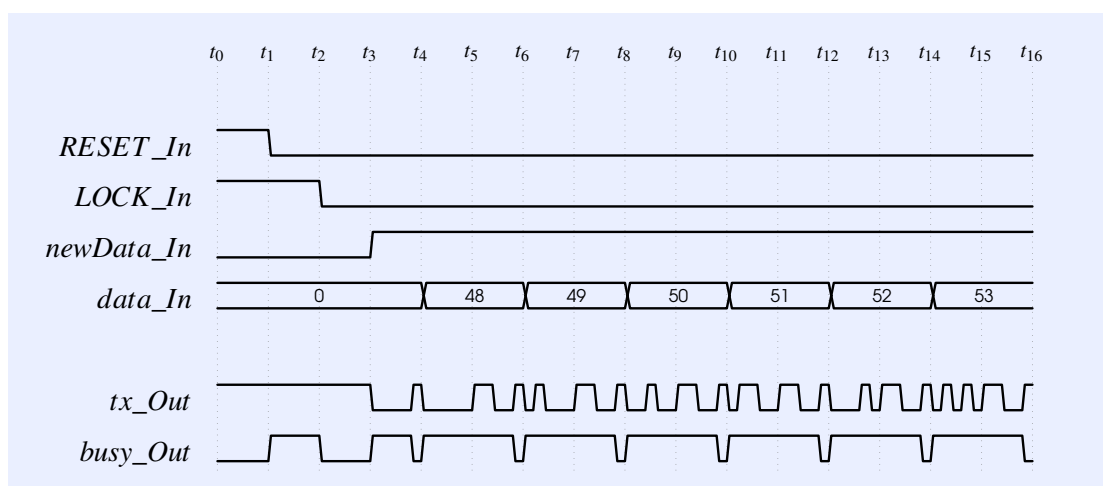Below is a diagram of what is expected to be obtained from the system. In this, despite the test vector layout includes an important quantity of bytes to transmit, the next diagram just cover a few data frames that exemplify the whole protocol procedure, which is the mayor purpose for this section.



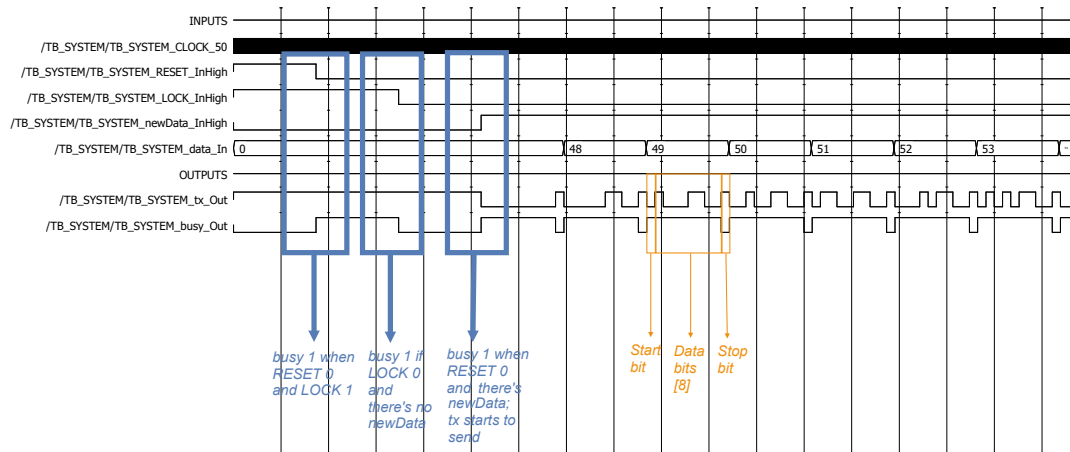On the other hand, the time diagram obtained in Altera's Quartus simulation tool is presented. In this case, we can check how it matches with what is expected. It is very important to highlight the sequential compound of this component, the 50MHz clock, which because of the very high frequency over the remaining signals, is depicted as a bold line.



1.1.14 Resource utilization

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student lists the resources used to build the module.

DELIVERABLES: A specific amount of resources in terms of quantity and percentage are presented.

- All the elements required for the module, as can be registers, logic gates and pins are enumerated. Besides, an explicit specification of the FPGA model used, is pointed out.

RESOURCE ELEMENT UTILIZATION		
Element	Amount	Percentage (Over total)
Logic gates	41	< 1%
Registers	30	-
Pins	14	9%
Device model	EP4CE22F17C6	
Family	Cyclone IV E	

1.1.15 Quartus diagrams

QUALITY PRODUCT:


PEDAGOGICAL OBJECTIVE: The student identifies elements of the Quartus Tool that can help the design process.

DELIVERABLES: Diagrams obtained in the tool.


- Diagrams obtained by Quartus are presented.



Block diagram

 

State machine diagram

 

1.1.16 Physical implementation

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student exposes a practical mode implementation to show the correct functionality of the core.

DELIVERABLES: Source codes and an abbreviated description of the way it was physically tested and the ports chosen as the I/O signals .

- The description is detailed at the point that can be recreated easily with the same features.
- All the source codes are included, even the ones detached to the HDL RTL codes.

To implement at physical level the serial communication transmitter, it was necessary to build another block shown below; this module is a counter, designed to increase by one as many times as a specific button is pressed. For this purpose, the total core had to be modified in terms of I/O signal ports and its connections between each other; the whole RTL source code can be consulted on the next online repository: https://github.com/favioacostad/UART_IP_Core/tree/main/PJRO_UART_TX/physical.

Additionally, the device which took the role of the peripheral receiver, was an Arduino Nano board; thanks to its connection to a computer, it was possible to check into the Arduino IDE, the byte size values coming from the FPGA port assigned to TX. Furthermore, throughout a set of eight LED's, all the coming data bytes could be corroborated. Finally, the reset and lock input signals, were allocated to a particular button as well.

```

1  /* #####
2  /** GOBIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  /** #####
4  /** Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /** Copyright (C) 2020. F.A. Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /**
7  /** This program is free software: you can redistribute it and/or modify
8  /** it under the terms of the GNU General Public License as published by
9  /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /** GNU General Public License for more details.
15 /**
16 /** You should have received a copy of the GNU General Public License
17 /** along with this program. If not, see <http://www.gnu.org/licenses/>
18 /** ##### */
19
20 //=====
21 // MODULE Definition
22 //=====
23 module PULSE_COUNTER #(parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 /////////////// OUTPUTS ///////////////
25     PULSE_COUNTER_newData_Out,
26     PULSE_COUNTER_data_Out,
27     PULSE_COUNTER_dataCounter_Out,
28 /////////////// INPUTS ///////////////
29     PULSE_COUNTER_CLOCK_50,
30     PULSE_COUNTER_RESET_InHigh,
31     PULSE_COUNTER_COUNT_InHigh,
32     PULSE_COUNTER_LOCK_InHigh,
33     PULSE_COUNTER_txBusy_InHigh
34 );

```



```
36 //=====
37 //  PARAMETER  Declarations
38 //=====
39 /////////////// STATES ///////////////
40 localparam    State_LOCK = 3'b000;
41 localparam    State_IDLE = 3'b001;
42 localparam    State_LOAD = 3'b010;
43 localparam    State_COUNT = 3'b011;
44
45 /////////////// SIZES ///////////////
46
47 //=====
48 //  PORT  Declarations
49 //=====
50 /////////////// OUTPUTS ///////////////
51 output        PULSE_COUNTER_newData_Out;
52 output [DATAWIDTH_BUS-1:0] PULSE_COUNTER_data_Out;
53 output [DATAWIDTH_BUS-1:0] PULSE_COUNTER_dataCounter_Out;
54 /////////////// INPUTS ///////////////
55 input         PULSE_COUNTER_CLOCK_50;
56 input         PULSE_COUNTER_RESET_InHigh;
57 input         PULSE_COUNTER_COUNT_InHigh;
58 input         PULSE_COUNTER_LOCK_InHigh;
59 input         PULSE_COUNTER_txBusy_InHigh;
60 /////////////// FLAGS ///////////////
61
62 //=====
63 //  REG/WIRE  Declarations
64 //=====
65 /////////////// REGISTERS ///////////////
66 // Boolean variable to inform of new data
67 reg NewData_Register;
68 // Data in terms of bytes
69 reg [DATAWIDTH_BUS-1:0] Data_Register;
70 // Current state of the protocol
71 reg [STATE_SIZE-1:0] State_Register;
72
73 /////////////// SIGNALS ///////////////
74 reg NewData_Signal;
75 reg [DATAWIDTH_BUS-1:0] Data_Signal;
76 reg [STATE_SIZE-1:0] State_Signal;
77
78 //=====
79 //  STRUCTURAL Coding
80 //=====
81 // INPUT LOGIC: Combinational
82 always @(*)
83 begin
84     case (State_Register)
85     State_LOCK:
86         if (PULSE_COUNTER_LOCK_InHigh)
87             State_Signal = State_LOCK;
88         else
89             State_Signal = State_IDLE;
90
91     State_IDLE:
92         if (~PULSE_COUNTER_COUNT_InHigh)
93             State_Signal = State_LOAD;
94         else
95             State_Signal = State_IDLE;
96
97     State_LOAD:
98         if (PULSE_COUNTER_COUNT_InHigh)
99             State_Signal = State_COUNT;
100        else
101            State_Signal = State_LOAD;
102
103     State_COUNT:
104         if (~PULSE_COUNTER_COUNT_InHigh & ~PULSE_COUNTER_txBusy_InHigh)
105             State_Signal = State_IDLE;
106         else
107             State_Signal = State_LOCK;
108
109     default: State_Signal = State_LOCK;
110     endcase
111 end
112
113 // STATE REGISTER : Sequential
114 always @(posedge PULSE_COUNTER_CLOCK_50, posedge PULSE_COUNTER_RESET_InHigh)
115 begin
116     if (PULSE_COUNTER_RESET_InHigh)
117     begin
118         NewData_Register <= 1'b0;
119         Data_Register <= {DATAWIDTH_BUS{1'b0}};
120         State_Register <= State_LOCK;
121     end
122
123     else
124     begin
125         NewData_Register <= NewData_Signal;
126         Data_Register <= Data_Signal;
127         State_Register <= State_Signal;
128     end
129 end
```




```
131 //=====
132 //  OUTPUTS
133 //=====
134 // OUTPUT LOGIC: Combinational
135 always @(*)
136 begin
137     case (State_Register)
138     State_LOCK:
139         begin
140             NewData_Signal = 1'b0;
141             Data_Signal = Data_Register;
142         end
143
144     State_IDLE:
145         begin
146             NewData_Signal = 1'b0;
147             Data_Signal = Data_Register;
148         end
149
150     State_LOAD:
151         begin
152             NewData_Signal = 1'b0;
153             Data_Signal = Data_Register;
154         end
155
156     State_COUNT:
157         begin
158             NewData_Signal = 1'b1;
159             Data_Signal = Data_Register + 8'b00000001;
160         end
161     endcase
162 end
163
164 // OUTPUT ASSIGNMENTS
165 assign PULSE_COUNTER_newData_Out = NewData_Register;
166 assign PULSE_COUNTER_data_Out = Data_Register;
167 assign PULSE_COUNTER_dataCounter_Out = Data_Register;
168
169 endmodule
```

Archive 1.5: PB_SYSTEM.v

1.1.17 Results and learnt lessons

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student discusses the design process identifying options for improvement and future work.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate and consistent).

- New specifications and applications of the work done (example: higher levels of complexity and uses in other contexts) are proposed.
- If the overall operating item is not achieved; identifies and argues the main reasons for non-functioning.
- Disciplinary language is accurate and appropriate, making use of grammatically correct phrases, without spelling errors.

The UART TX transmitter is one of the most simple protocols to send data. As a matter of fact, last allows lower processing requirements and increases the upper speed limits in terms of the baud rate. Furthermore, thanks to the configuration set for this protocol, the communication is Full Duplex, which allows to send and receive data with a peripheral device simultaneously.

The data frame can contain a bit parity detection error as well, nevertheless, for this application, this is not took into account. Last, to avoid losing compatibility with an important amount of devices.



1.2 Receptor (RX)

Below, the serial communication component **UART Receptor (RX)** is presented, showing its protocol to receive information. To consult the whole UART receptor core and its source codes, the next repository link can be followed: https://github.com/favioacostad/UART_IP_Core/tree/main/PJRO_UART_RX

1.2.1 Component description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student understands and proposes product specifications and restrictions.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate, and consistent) that explain: constraints, specifications, and search and identification of contexts where that component is used.

- a. The description of the component is written in the student words, organized logically and clearly.
- b. The specifications and restrictions fully respond to the requested component, demonstrating originality and own contributions.
- c. The search and identification of contexts where this component is used is clear.
- d. Discipline language is accurate and appropriate, phrases are grammatically correct and there are no spelling errors.

The serial receptor port for UART is a module that, together with the transmitter, has been positioned as one of the most common Serial Communication Protocol among peripherals and devices, which can be focused on different fields. In this component, because of the asynchronous feature, is necessary to establish a baud (Bits/Sec) rate as an agreement of both terminals. Equally relevant, is the data frame configuration with 1 *start bit* at low level, followed by the 8 *data bits* and the *stop bit* at high level.

Henceforth, the protocol's state will be **Idle** until the start bit appears with a low level signal. Additionally, the algorithm developed for this module was proposed to read on its middle, the bit value coming through the **rx** port. To put it in other words, the moment when the receptor takes the data value, is computed as a half number of clock cycles each binary digit cover; last cycles are designated in the **Clock per bit** parameter. In turns, this parameter depends of the ratio between the Frequency processing and the Baud rate established.


1.2.2 Symbol

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates his component to a generic symbol usable in an architectural diagram.

DELIVERABLES: Correct and complete diagram.

 - a. The symbol proposed to represent the component is based on symbols of a similar nature presented in the electronic component literature.



1.2.3 Port description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student recognizes all the Input/Output (I/O) ports the module has.

DELIVERABLES: A description of each I/O port signal where its type, size and initial state are enunciated.

- The whole I/O signal ports are explicitly described and it is easy to understand the functionality for each one into the core.
- It is clear for the input ports, what kind of signal has to be stimulated to get a correct performance.

I/O Ports description				
Name	Signal type	Size	Initial state	Description
BB_SYSTEM_newData_Out	Output	1	0	Boolean signal to inform of new data to an external module.
BB_SYSTEM_data_Out	Output	8	00000000	Data in terms of bytes ready to process.
BB_SYSTEM_CLOCK_50	Input	1	-	Clock of the system with a default value of 50MHz.
BB_SYSTEM_RESET_InHigh	Input	1	0	Reset signal in case of reload the initial values for the module.
BB_SYSTEM_LOCK_InHigh	Input	1	0	Boolean signal to lock or not the module from an external signal.
BB_SYSTEM_rx_InLow	Input	1	1	Receiver signal in charge of getting the data from the transmitter based on the baud rate.


1.2.4 Black box diagram

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies input/output signals for the product.

DELIVERABLES: Correct and complete diagram.

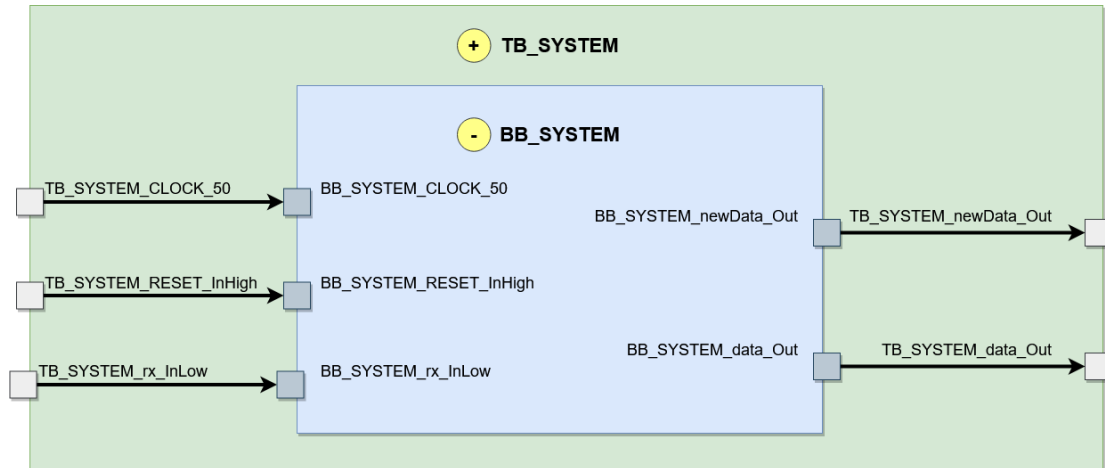- There is full correspondence between the black box diagram and the functionality of the requested component.
- The black box diagram shows all input and output signals with their corresponding structured names (In/Out) and sizes (bit/bus).
- The black box diagram relates that component to the characterization diagram (test-bench).



1.2.5 Functionality

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student breaks down the problem into a set of steps that respond to the expected functionality.

DELIVERABLES: Equation / Truth Table / Macro-algorithm correct and complete according to component functionality.

- The character equation and/or truth table and/or solution macro-algorithm correctly describes the functionality of the component and is properly represented by a detailed explanation where each step is less complex than the requested component.



Characteristic equation

$$\begin{aligned}
 (rx_In)_{CLOCK_PER_BIT} &\leq data_In[0] \\
 (rx_In)_{CLOCK_PER_BIT} &\leq data_In[1] \\
 &\dots \\
 (rx_In)_{CLOCK_PER_BIT} &\leq data_In[7]
 \end{aligned}$$



Truth table

INPUTS		OUTPUTS	
RESET_In	rx_In	newData_Out	data_Out
1	0	0	00000000
1	1	0	00000000
0	1	0	00000000
0	0	0	00000000
0	1	0	00000000
0	1	0	00000001
0	1	0	00000011
0	0	0	00000111
0	1	0	00001110
0	0	0	00011101
0	1	0	00111010
0	0	0	01110101
0	1	1	11101010

**Macro-algorithm****Algorithm 3: Receptor port RX****Data:***RESET_In, rx_In***Algorithm:***newData_Out = 0**data_Out = 00000000**counter = 0**counterBit = 0**CLOCK_PER_BIT = Freq/BaudRate**if not RESET_In:**case state:**IDLE:**if not rx_In:**state = WAIT_HALF**WAIT_HALF:**counter += 1**if counter == CLOCK_PER_BIT/2:**counter = 0**state = WAIT_FULL_INIT**WAIT_FULL_INIT:**counter += 1**if counter == CLOCK_PER_BIT:**counter = 0**state = WAIT_FULL_END**WAIT_FULL_END:**newData_Out = 1**data_Out = [rx_In, data_Out[7:1]]**counterBit += 1**if counterBit == 7:**counterBit = 0**counter = 0**state = WAIT_HIGH**else:**state = WAIT_FULL_INIT**WAIT_HIGH:**if rx_In:**state = IDLE**end case***Results:***newData_Out, [7:0] data_Out*



1.2.6 Reference model

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student proposes a reference model as function verification and control verification of RTL models, which can be constructed with software high level languages like C, C++, JavaScript, Python, etc.

DELIVERABLES: Source codes.

- The description in software language has similar structure to the hardware language algorithm.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.
- The validation model verifies the consistency of the RTL modules by judging whether the two designs are equivalent and consistent.

The source code below, just depicts the function based on the UART White Box module for reception. To consult the whole reference model, it is necessary to visit the next on-line repository: https://github.com/favioacostad/UART_IP_Core/tree/main/PJR0_UART_RX/reference.

```

1  #=====
2  # LIBRARIES Definition
3  #=====
4  # Libraries required along the code
5  import numpy as np
6  np.set_printoptions(threshold = np.inf)
7
8  #=====
9  # MODULE Definition
10 #=====
11 # Function describing UART serial communication protocol for reception
12 def UART_RX (UART_RX_CLOCK_50, UART_RX_RESET_InHigh, UART_RX_rx_InLow,
13              CLOCK_PER_BIT, DATAWIDTH_BUS, STATE_SIZE):
14
15     #=====
16     # PARAMETER Declarations
17     #=====
18     #//////////////// STATES //////////////////
19     State_IDLE = np.uint8(0)
20     State_WAIT_HALF = np.uint8(1)
21     State_WAIT_FULL_INIT = np.uint8(2)
22     State_WAIT_FULL_END = np.uint8(3)
23     State_WAIT_HIGH = np.uint8(4)
24     #//////////////// SIZES //////////////////
25     # Ceiling of log base 2 to get the number of bits needed to store a value
26     # CLOCK_PER_BIT = 50MHz/256000Bauds
27     COUNTER_SIZE = int(np.log2(CLOCK_PER_BIT)) # 8 bits
28
29     #=====
30     # PORT Declarations
31     #=====
32     #//////////////// OUTPUTS //////////////////
33     # Default values
34     UART_RX_newData_Out = np.uint8(1)
35     UART_RX_data_Out = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
36
37     #=====
38     # REG/WIRE Declarations
39     #=====
40     # Registers (Q)
41     global NewData_Register, Data_Register, Rx_Register, State_Register
42     global Counter_Register, BitCounter_Register
43
44     #=====
45     # STRUCTURAL Coding
46     #=====
47     # INPUT LOGIC: Combinational
48     # Signals (D)
49     Rx_Signal = UART_RX_rx_InLow
50     State_Signal = State_Register
51     Counter_Signal = Counter_Register
52     BitCounter_Signal = BitCounter_Register
53
54     if State_Register == State_IDLE:
55         Counter_Signal = 0
56         BitCounter_Signal = 0
57         if Rx_Register == np.uint8(0):
58             State_Signal = State_WAIT_HALF
59         else:
60             State_Signal = State_IDLE
61
62     elif State_Register == State_WAIT_HALF:
63         Counter_Signal = Counter_Register + 1
64         # The counter is compared with half of the CLOCK_PER_BIT
65         if Counter_Register == (CLOCK_PER_BIT >> np.uint8(1)):
66             State_Signal = State_WAIT_FULL_INIT
67             Counter_Signal = 0
68         else:
69             State_Signal = State_WAIT_HALF

```



```
71 elif State_Register == State_WAIT_FULL_INIT:
72     Counter_Signal = Counter_Register + 1
73     if Counter_Register == CLOCK_PER_BIT-1:
74         State_Signal = State_WAIT_FULL_END
75         Counter_Signal = 0
76     else:
77         State_Signal = State_WAIT_FULL_INIT
78
79 elif State_Register == State_WAIT_FULL_END:
80     BitCounter_Signal = BitCounter_Register + 1
81     if BitCounter_Register == DATAWIDTH_BUS-1:
82         State_Signal = State_WAIT_HIGH
83         Counter_Signal = 0
84     else:
85         State_Signal = State_WAIT_FULL_INIT
86
87 elif State_Register == State_WAIT_HIGH:
88     Counter_Signal = Counter_Register + 1
89     if Rx_Register == np.uint8(1):
90         State_Signal = State_IDLE
91         Counter_Signal = 0
92     else:
93         State_Signal = State_WAIT_HIGH
94
95 else:
96     State_Signal = State_IDLE
97
98 #=====
99 # OUTPUTS
100 #=====
101 # OUTPUT LOGIC: Combinational
102 # Signals (D)
103 NewData_Signal = NewData_Register
104
105 if State_Register == State_IDLE:
106     NewData_Signal = np.uint8(0)
107     Data_Signal = Data_Register
108
109 elif State_Register == State_WAIT_HALF:
110     NewData_Signal = np.uint8(0)
111     Data_Signal = Data_Register
112
113 elif State_Register == State_WAIT_FULL_INIT:
114     NewData_Signal = np.uint8(0)
115     Data_Signal = Data_Register
116
117 elif State_Register == State_WAIT_FULL_END:
118     NewData_Signal = np.uint8(1)
119     Data_Signal = np.array([Data_Register[i] for i in range(1,8)])
120     Data_Signal = np.insert(Data_Signal,7,Rx_Register,axis = 0)
121
122 elif State_Register == State_WAIT_HIGH:
123     NewData_Signal = np.uint8(0)
124     Data_Signal = Data_Register
125
126 else:
127     NewData_Signal = np.uint8(0)
128     Data_Signal = Data_Register
129
130 # STATE REGISTER : Sequential
131 if UART_RX_CLOCK_50:
132     # Updating global registers
133     if UART_RX_RESET_InHigh:
134         NewData_Register = np.uint8(0)
135         Data_Register = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
136         Rx_Register = np.uint8(1)
137         State_Register = State_IDLE
138         Counter_Register = 0
139         BitCounter_Register = 0
140     else:
141         NewData_Register = NewData_Signal
142         Data_Register = Data_Signal
143         Rx_Register = Rx_Signal
144         State_Register = State_Signal
145         Counter_Register = Counter_Signal
146         BitCounter_Register = BitCounter_Signal
147
148 # OUTPUT ASSIGNMENTS
149 UART_RX_newData_Out = NewData_Register
150 UART_RX_data_Out = Data_Register
151
152 return UART_RX_newData_Out, UART_RX_data_Out
```

Archive 1.6: REF_SYSTEM.py



1.2.7 HDL: Black box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* #####
2  /** GOBIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  /** #####
4  /** Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /** Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /**
7  /** This program is free software: you can redistribute it and/or modify
8  /** it under the terms of the GNU General Public License as published by
9  /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /** GNU General Public License for more details.
15 /**
16 /** You should have received a copy of the GNU General Public License
17 /** along with this program. If not, see <http://www.gnu.org/licenses/>
18 /** ##### */

20 //=====
21 // MODULE Definition
22 //=====
23 module BB_SYSTEM (
24 // ===== OUTPUTS =====
25     BB_SYSTEM_newData_Out,
26     BB_SYSTEM_data_Out,
27 // ===== INPUTS =====
28     BB_SYSTEM_CLOCK_50,
29     BB_SYSTEM_RESET_InHigh,
30     BB_SYSTEM_rx_InLow
31 );

33 //=====
34 // PARAMETER Declarations
35 //=====
36 // ===== BAUD RATE =====
37 // Ratio between the internal frequency and the baud rate
38 parameter CLOCK_PER_BIT = 434; // CLOCK_PER_BIT = 50MHz/115200Bauds
39 //parameter CLOCK_PER_BIT = 868; // CLOCK_PER_BIT = 50MHz/57600Bauds
40 //parameter CLOCK_PER_BIT = 2604; // CLOCK_PER_BIT = 50MHz/19200Bauds
41 //parameter CLOCK_PER_BIT = 5208; // CLOCK_PER_BIT = 50MHz/9600Bauds
42 // ===== SIZES =====
43 // Data width of the input bus
44 parameter DATAWIDTH_BUS = 8;
45 // Size for the states needed into the protocol
46 parameter STATE_SIZE = 3;

48 //=====
49 // PORT Declarations
50 //=====
51 // ===== OUTPUTS =====
52 output BB_SYSTEM_newData_Out;
53 output [DATAWIDTH_BUS-1:0] BB_SYSTEM_data_Out;
54 // ===== INPUTS =====
55 input BB_SYSTEM_CLOCK_50;
56 input BB_SYSTEM_RESET_InHigh;
57 input BB_SYSTEM_rx_InLow;

59 //=====
60 // REG/WIRE Declarations
61 //=====

63 //=====
64 // STRUCTURAL Coding
65 //=====
66 UART_RX #(CLOCK_PER_BIT(CLOCK_PER_BIT), .DATAWIDTH_BUS(DATAWIDTH_BUS), .STATE_SIZE(STATE_SIZE)) UART_RX_u0 (
67 // Port map - connection between master ports and signals/registers
68 // ===== OUTPUTS =====
69     .UART_RX_newData_Out(BB_SYSTEM_newData_Out),
70     .UART_RX_data_Out(BB_SYSTEM_data_Out),
71 // ===== INPUTS =====
72     .UART_RX_CLOCK_50(BB_SYSTEM_CLOCK_50),
73     .UART_RX_RESET_InHigh(BB_SYSTEM_RESET_InHigh),
74     .UART_RX_rx_InLow(BB_SYSTEM_rx_InLow)
75 );

77 endmodule

```

Archive 1.7: BB_SYSTEM.v



1.2.8 Test vector definition

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student proposes a strategy to validate the functionality of the product.

DELIVERABLES: Clear selection strategies. Clear explanation of operation.

- a. Test vectors are selected by describing an explicit and clearly defined strategy in a paragraph, and these vectors allow you to fully verify functionality.

The test vectors are composed first, by the reset input and second, by the RX input. The last port with the vital duty of carry the information sent by the source device. With the purpose of simulate practice related situations, the byte values for testing were chosen from the ASCII (American Standard Code for Information Interchange) to recreate character transmission.

TEST VECTOR INPUTS	
RESET_In	rx_In
1	1
0	1
0	0
0	0
0	1
0	0
0	1
0	0
0	1
0	1
0	0
0	1
0	1
0	1

1.2.9 HDL: Test vectors

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- a. The description in hardware languages is correct and corresponds to the requested component.
- b. Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```
1 /* *****
2 2 // G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3 3 // *****
4 4 // Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5 5 // Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6 6 //
7 7 // This program is free software: you can redistribute it and/or modify
8 8 // it under the terms of the GNU General Public License as published by
9 9 // the Free Software Foundation, version 3 of the License.
10 10 //
11 11 // This program is distributed in the hope that it will be useful,
12 12 // but WITHOUT ANY WARRANTY; without even the implied warranty of
13 13 // MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 14 // GNU General Public License for more details.
15 15 //
16 16 // You should have received a copy of the GNU General Public License
17 17 // along with this program. If not, see <http://www.gnu.org/licenses/>
18 18 // ***** */
19
20 // =====
21 // MODULE Definition
22 // =====
23 // Escala de tiempo
```



```
24 `timescale 1 ns / 1 ns
25 module TB_SYSTEM();
26 // Constants
27 //=====
28 // Parameter (May differ for physical synthesis)
29 //=====
30 // General purpose registers
31 reg eachvec;
32 parameter TCK = 20; // Clock period in ns
33 parameter CLK_FREQ = 1000000000 / TCK; // Frequency in HZ
34 parameter DATAWIDTH_BUS = 8;
35 parameter CLOCK_PER_BIT = 434; // CLOCK_PER_BIT = 50MHz/115200 Bauds
36 //parameter CLOCK_PER_BIT = 868; // CLOCK_PER_BIT = 50MHz/57600 Bauds
37 //parameter CLOCK_PER_BIT = 2604; // CLOCK_PER_BIT = 50MHz/19200 Bauds
38 //parameter CLOCK_PER_BIT = 5208; // CLOCK_PER_BIT = 50MHz/9600 Bauds
39
40 // Test vector input registers
41
42 //=====
43 // INTERNAL WIRE/REG Declarations
44 //=====
45 // Wires (OUTPUTS)
46 wire TB_SYSTEM_newData_Out;
47 wire [DATAWIDTH_BUS-1:0] TB_SYSTEM_data_Out;
48 // Reg (INPUTS)
49 reg TB_SYSTEM_CLOCK_50;
50 reg TB_SYSTEM_RESET_InHigh;
51 reg TB_SYSTEM_rx_InLow;
52
53 // Assign statements (If any)
54 BB_SYSTEM BB_SYSTEM_u0 (
55 // Port map - connection between master ports and signals/registers
56 /////////////// OUTPUTS ///////////////////
57 .BB_SYSTEM_newData_Out(TB_SYSTEM_newData_Out) ,
58 .BB_SYSTEM_data_Out(TB_SYSTEM_data_Out) ,
59 /////////////// INPUTS ///////////////////
60 .BB_SYSTEM_CLOCK_50(TB_SYSTEM_CLOCK_50) ,
61 .BB_SYSTEM_RESET_InHigh(TB_SYSTEM_RESET_InHigh) ,
62 .BB_SYSTEM_rx_InLow(TB_SYSTEM_rx_InLow)
63 );
64
65 initial
66 begin
67 // Code that executes only once
68 // Insert code here --> begin
69 TB_SYSTEM_CLOCK_50 <= 0;
70 // --> end
71 $display("Running testbench");
72 end
73
74 always
75 // Optional sensitivity list
76 // @(Event1 or event2 or .... eventn)
77 #(TCK/2) TB_SYSTEM_CLOCK_50 <= ~ TB_SYSTEM_CLOCK_50;
78
79 initial begin
80 // Code executes for every event on sensitivity list
81 // Insert code here --> begin
82
83 #0 TB_SYSTEM_RESET_InHigh <= 1'b1; TB_SYSTEM_rx_InLow <= 1'b0;
84
85 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
86 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
87
88 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
89 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
90 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
91 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
92 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
93 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
94 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
95 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
96
97 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
98
99 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
100 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
101 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
102
103 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
104 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
105 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
106 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
107 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
108 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
109 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
110 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
111
112 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
113
114 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
115 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
116 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
117 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
118 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
```



```

119
120 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
121 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
122 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
123 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
124 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
125 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
126 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
127 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
128
129 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
130
131 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
132 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
133 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
134 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
135 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
136 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
137 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
138 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
139 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
140
141 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
142 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
143 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
144 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
145 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
146 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
147 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
148 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b0;
149
150 #(TCK*CLOCK_PER_BIT) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_rx_InLow <= 1'b1;
151
152 // #(TCK*10000) $finish;
153 @eachvec;
154 $finish;
155 // --> end
156 end
157 endmodule

```

Archive 1.8: TB_SYSTEM.vt

1.2.10 White box diagram


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student makes a diagram of sub-components, signals and interconnections and makes a description of each sub-component.

DELIVERABLES: Diagram of sub-components, signals and interconnections, description of component or component to component.

- The white box diagram is correct and corresponds to the requested component.
- All internal and input/output signals with their corresponding structured names (In/Out) and sizes (Bit/Bus) are displayed for all internal system components.
- The white box diagram corresponds to an efficient solution in terms of resources, number of blocks and elements and solution algorithm. Internal components are less complex than those with higher hierarchy.
- A description (what is and how it works) of each of the constituent components of the requested component is presented, describing its signals.

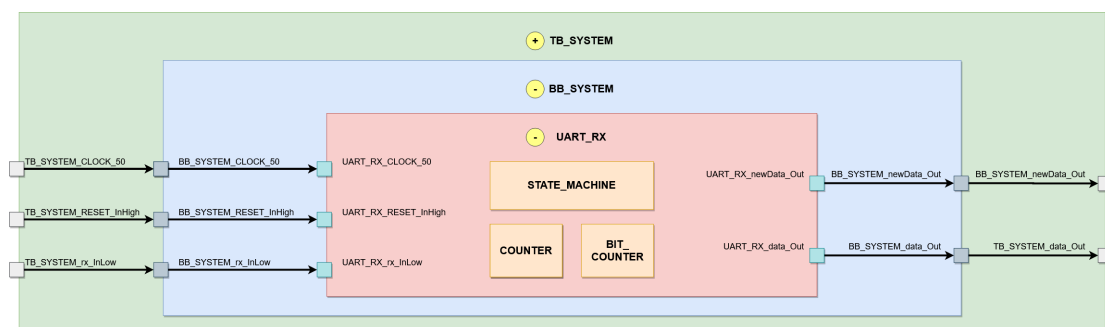For this specific case, the input/output ports match with the higher module into the hierarchical design.





1.2.11 HDL: White box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* #####
2  /** G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  #####
4  /** Copyright (C) 2018, F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /** Copyright (C) 2020, F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /**
7  /** This program is free software: you can redistribute it and/or modify
8  /** it under the terms of the GNU General Public License as published by
9  /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /** GNU General Public License for more details.
15 /**
16 /** You should have received a copy of the GNU General Public License
17 /** along with this program. If not, see <http://www.gnu.org/licenses/>
18 /** ##### */

20 //=====
21 // MODULE Definition
22 //=====
23 module UART_RX #(parameter CLOCK_PER_BIT, parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 /////////////// OUTPUTS ///////////////////
25     UART_RX_newData_Out,
26     UART_RX_data_Out,
27 /////////////// INPUTS ///////////////////
28     UART_RX_CLOCK_50,
29     UART_RX_RESET_InHigh,
30     UART_RX_rx_InLow
31 );

33 //=====
34 // PARAMETER Declarations
35 //=====
36 /////////////// STATES ///////////////////
37 localparam State_IDLE = 3'b000;
38 localparam State_WAIT_HALF = 3'b001;
39 localparam State_WAIT_FULL_INIT = 3'b010;
40 localparam State_WAIT_FULL_END = 3'b011;
41 localparam State_WAIT_HIGH = 3'b100;
42 /////////////// SIZES ///////////////////
43 // Ceiling of log base 2 to get the number of bits needed to store a value
44 // CLOCK_PER_BIT = 50MHz/115200Bauds
45 localparam COUNTER_SIZE = $clog2(CLOCK_PER_BIT); // 8 bits

47 //=====
48 // PORT Declarations
49 //=====
50 /////////////// OUTPUTS ///////////////////
51 output UART_RX_newData_Out;
52 output [DATAWIDTH_BUS-1:0] UART_RX_data_Out;
53 /////////////// INPUTS ///////////////////
54 input UART_RX_CLOCK_50;
55 input UART_RX_RESET_InHigh;
56 input UART_RX_rx_InLow;
57 /////////////// FLAGS ///////////////////

59 //=====
60 // REG/WIRE Declarations
61 //=====
62 /////////////// REGISTERS ///////////////////
63 // Boolean variable to inform of new data
64 reg NewData_Register;
65 // Data in terms of bytes
66 reg [DATAWIDTH_BUS-1:0] Data_Register;
67 // Receptor
68 reg Rx_Register;
69 // Current state of the protocol
70 reg [STATE_SIZE-1:0] State_Register;
71 // Counter for the clock cycles carried out so far
72 reg [COUNTER_SIZE-1:0] Counter_Register;
73 // Counter for the number of bits carried out so far
74 reg [2:0] BitCounter_Register;
75 /////////////// SIGNALS ///////////////////
76 reg NewData_Signal;
77 reg [DATAWIDTH_BUS-1:0] Data_Signal;
78 reg Rx_Signal;
79 reg [STATE_SIZE-1:0] State_Signal;
80 reg [COUNTER_SIZE-1:0] Counter_Signal;

```



```
81 reg [2:0] BitCounter_Signal;
82
83 //=====
84 // STRUCTURAL Coding
85 //=====
86 // INPUT LOGIC: Combinational
87 always @(*)
88 begin
89     // To init registers
90     // State_Signal = State_Register;
91     Rx_Signal = UART_RX_rx_InLow;
92     Counter_Signal = Counter_Register;
93     BitCounter_Signal = BitCounter_Register;
94
95     case (State_Register)
96     State_IDLE:
97         begin
98             Counter_Signal = {COUNTER_SIZE{1'b0}};
99             BitCounter_Signal = 3'b000;
100             if (Rx_Register)
101                 State_Signal = State_IDLE;
102             else
103                 State_Signal = State_WAIT_HALF;
104         end
105
106     State_WAIT_HALF:
107         begin
108             Counter_Signal = Counter_Register + 1'b1;
109             if (Counter_Register == (CLOCK_PER_BIT >> 1))
110                 begin
111                     State_Signal = State_WAIT_FULL_INIT;
112                     Counter_Signal = {COUNTER_SIZE{1'b0}};
113                 end
114             else
115                 State_Signal = State_WAIT_HALF;
116         end
117
118     State_WAIT_FULL_INIT:
119         begin
120             Counter_Signal = Counter_Register + 1'b1;
121             if (Counter_Register == CLOCK_PER_BIT-1)
122                 begin
123                     State_Signal = State_WAIT_FULL_END;
124                     Counter_Signal = {COUNTER_SIZE{1'b0}};
125                 end
126             else
127                 State_Signal = State_WAIT_FULL_INIT;
128         end
129
130     State_WAIT_FULL_END:
131         begin
132             BitCounter_Signal = BitCounter_Register + 1'b1;
133             if (BitCounter_Register == DATAWIDTH_BUS-1)
134                 begin
135                     State_Signal = State_WAIT_HIGH;
136                     Counter_Signal = {COUNTER_SIZE{1'b0}};
137                     BitCounter_Signal = 3'b000;
138                 end
139             else
140                 State_Signal = State_WAIT_FULL_INIT;
141         end
142
143     State_WAIT_HIGH:
144         begin
145             if (Rx_Register)
146                 State_Signal = State_IDLE;
147             else
148                 State_Signal = State_WAIT_HIGH;
149         end
150
151     default: State_Signal = State_IDLE;
152     endcase
153 end
154
155 // STATE REGISTER : Sequential
156 always @(posedge UART_RX_CLOCK_50, posedge UART_RX_RESET_InHigh)
157 begin
158     if (UART_RX_RESET_InHigh)
159         begin
160             NewData_Register <= 1'b0;
161             Data_Register <= {DATAWIDTH_BUS{1'b0}};
162             Rx_Register <= 1'b1;
163             State_Register <= State_IDLE;
164             Counter_Register <= {COUNTER_SIZE{1'b0}};
165             BitCounter_Register <= 3'b000;
166         end
167
168     else
169         begin
170             NewData_Register <= NewData_Signal;
171             Data_Register <= Data_Signal;
172             Rx_Register <= Rx_Signal;
173             State_Register <= State_Signal;
174             Counter_Register <= Counter_Signal;
175             BitCounter_Register <= BitCounter_Signal;
```



```
176     end
177 end
178
179 //=====
180 //  OUTPUTS
181 //=====
182 // OUTPUT LOGIC: Combinational
183 always @(*)
184 begin
185     // To init registers
186     case (State_Register)
187     State_IDLE:
188         begin
189             NewData_Signal = 1'b0;
190             Data_Signal = Data_Register;
191         end
192
193     State_WAIT_HALF:
194         begin
195             NewData_Signal = 1'b0;
196             Data_Signal = Data_Register;
197         end
198
199     State_WAIT_FULL_INIT:
200         begin
201             NewData_Signal = 1'b0;
202             Data_Signal = Data_Register;
203         end
204
205     State_WAIT_FULL_END:
206         begin
207             NewData_Signal = 1'b1;
208             Data_Signal = {Rx_Register, Data_Register[7:1]};
209         end
210
211     State_WAIT_HIGH:
212         begin
213             NewData_Signal = 1'b0;
214             Data_Signal = Data_Register;
215         end
216
217     default:
218         begin
219             NewData_Signal = 1'b0;
220             Data_Signal = Data_Register;
221         end
222     endcase
223 end
224
225 // OUTPUT ASSIGNMENTS
226 assign UART_RX_newData_Out = NewData_Register;
227 assign UART_RX_data_Out = Data_Register;
228
229 endmodule
```

Archive 1.9: WB_SYSTEM.v

1.2.12 HDL: Blocks

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

From this particular case, there's no elements of lower hierarchy.

1.2.13 Temporal simulation

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates the functionality according to the proposed specifications with various types of tests.


DELIVERABLES: Functionality according to the proposed specifications and in various types of tests.

- Simulation results are presented for the requested product, explaining three or more operating cases on the simulation diagram. The simulation contains markers on the graph that indicate specific situations of the prototype.


Below is a diagram of what is expected to be obtained from the system. In this, despite the



 test vector layout includes a bunch of bytes to transmit, the next diagram just cover one data frame that exemplifies the whole protocol procedure, which is the mayor purpose for this section. With this intention, the character 'j' (01101010) on binary or (106) on decimal base is tested.



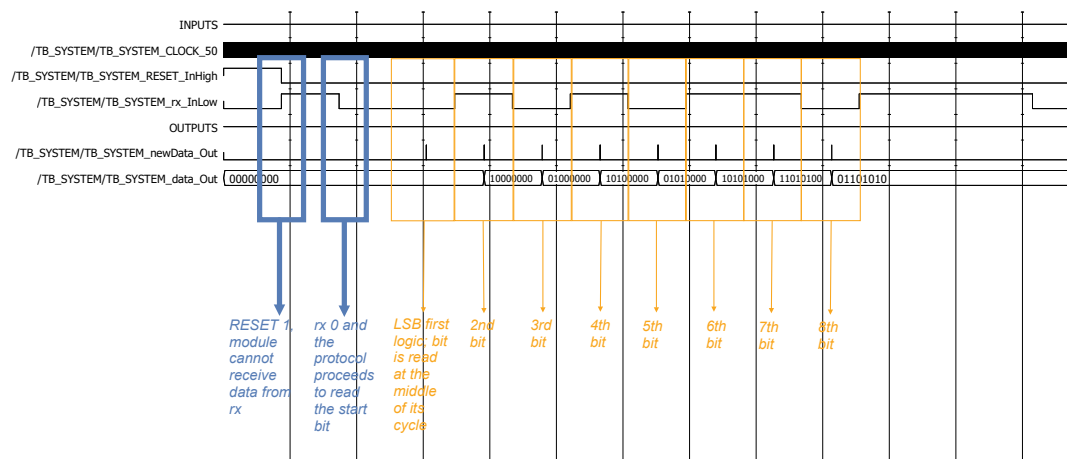On the other hand, the time diagram obtained in Altera's Quartus simulation tool is presented. In this case, we can check how it matches with what is expected. It is very important to highlight the sequential compound of this component, the 50MHz clock, which because of the very high frequency over the remaining signals, is depicted as a bold line.



1.2.14 Resource utilization

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student lists the resources used to build the module.

DELIVERABLES: A specific amount of resources in terms of quantity and percentage are presented.

- All the elements required for the module, as can be registers, logic gates and pins are enumerated. Besides, an explicit specification of the FPGA model used, is pointed out.

RESOURCE ELEMENT UTILIZATION		
Element	Amount	Percentage (Over total)
Logic gates	38	< 1%
Registers	27	-
Pins	12	8%
Device model	EP4CE22F17C6	
Family	Cyclone IV E	



1.2.15 Quartus diagrams


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies elements of the Quartus Tool that can help the design process.


DELIVERABLES: Diagrams obtained in the tool.

- Diagrams obtained by Quartus are presented.

Block diagram

 

State machine diagram

 

1.2.16 Physical implementation

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student exposes a practical mode implementation to show the correct functionality of the core.

DELIVERABLES: Source codes and an abbreviated description of the way it was physically tested and the ports chosen as the I/O signals .

- The description is detailed at the point that can be recreated easily with the same features.
- All the source codes are included, even the ones detached to the HDL RTL codes.

To implement at physical level the serial communication receiver, it wasn't necessary to build another block; in fact, the total core hadn't to be modified in terms of I/O signal ports. Now, the device which took the role of the peripheral transmitter, was an Arduino Nano board; thanks to its connection to a computer, it was possible to check into the Arduino IDE, the byte size values sent to the FPGA port assigned to RX. Furthermore, throughout a set of eight LED's, all the coming data bytes could be corroborated. Finally, the reset input signal, were allocated to a particular button as well.

The Arduino source code used to carry out the physical implementation can be found into the next online repository: https://github.com/favioacostad/UART_IP_Core/tree/main/PJRO_UART_RX/rtl.



1.2.17 Results and learnt lessons

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student discusses the design process identifying options for improvement and future work.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate and consistent).

- a. New specifications and applications of the work done (example: higher levels of complexity and uses in other contexts) are proposed.
- b. If the overall operating item is not achieved; identifies and argues the main reasons for non-functioning.
- c. Disciplinary language is accurate and appropriate, making use of grammatically correct phrases, without spelling errors.

In spite of the simplicity of the RX protocol, is widely applied thanks to the reduced processing requirements and the low probability of being prone to errors. In fact, last feature, although it depends of other conditions (i.e. distance length), is relatively low; under these circumstances, the data frame with bit parity detection is considered useless for a larger part of device designers.

UART communication protocol, thanks to its supporting of low rates, to send and receive data, can be more practical for some applications over other synchronous serial protocols. However, in terms of high speed rates, there's a disadvantage in relation with SPI or IC that can tolerate up to 25Mbps and 1Mbps respectively; in comparison, UART limit is close to 2.5Kbps.

2. Serial Peripheral Interface (SPI).

Peter Drucker

The most important thing in communication
is hearing what isn't said.

Components designed:

Along this chapter, the synchronous serial communication protocol SPI will be exposed, showing the master (M) block and the slave block (S) with its specific features governed by the protocol definition.

2.1 Master (M)

Below, the serial communication component **SPI Master (M)** is presented, showing its protocol to receive and to send information. To consult the whole SPI master core and its source codes, the next repository link can be followed: https://github.com/favioacostad/SPI_IP_Core/tree/main/PJRO_SPI_MASTER

2.1.1 Component description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student understands and proposes product specifications and restrictions.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate, and consistent) that explain: constraints, specifications, and search and identification of contexts where that component is used.

- The description of the component is written in the student words, organized logically and clearly.
- The specifications and restrictions fully respond to the requested component, demonstrating originality and own contributions.
- The search and identification of contexts where this component is used is clear.
- Discipline language is accurate and appropriate, phrases are grammatically correct and there are no spelling errors.

The master module for SPI is a block extensively used into the System on Chip (SoC) communication field to transmit information between devices. It has a synchronous feature, which means that all the functionality and the state machine is based on a clock usually in a range of MHz. Regarding the data frame format sent by the module through the Master Out Slave In (**MOSI**) port, there's an idle state where this signal takes a logic value of 1; then, depending on the rise/fall edge of the Slave Clock (**SCK**), the 8 data bits are transmitted. These data is



required to send by an external module that informs of this task by sending a Boolean signal **Start**.


It is relevant to mention the different working modes for this protocol which can variate with the Clock Polarity (**CPOL**) and the Clock Phase (**CPHA**). Specifically, there's 4 standard modes where **CPOL** and **CPHA** can take two values 0 or 1 and designate if the **SCK** idle value is in High (**CPOL = 1**) or Low (**CPOL = 0**) state; in the same way, to indicate whether the edge for this clock is chosen to sample with rise and transmit with fall (**CPHA = 1**) or sample with fall and transmit with rise (**CPHA = 10**).

2.1.2 Symbol

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates his component to a generic symbol usable in an architectural diagram.
DELIVERABLES: Correct and complete diagram.

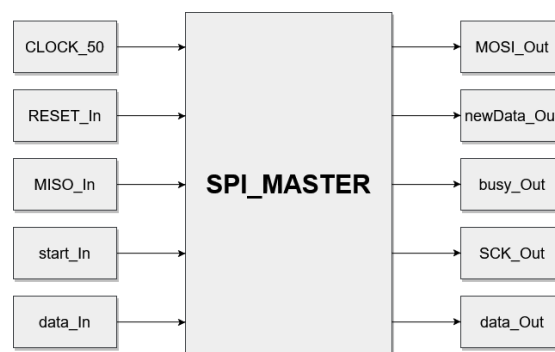- The symbol proposed to represent the component is based on symbols of a similar nature presented in the electronic component literature.



2.1.3 Port description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student recognizes all the Input/Output (I/O) ports the module has.
DELIVERABLES: A description of each I/O port signal where its type, size and initial state are enunciated.

- The whole I/O signal ports are explicitly described and it is easy to understand the functionality for each one into the core.
- It is clear for the input ports, what kind of signal has to be stimulated to get a correct performance.



I/O Ports description				
Name	Signal type	Size	Initial state	Description
BB_SYSTEM_MOSI_Out	Output	1	1	Transmitter signal in charge of carrying the data to the slave based on the clock ratio set.
BB_SYSTEM_newData_Out	Output	1	0	Boolean signal to inform of new data ready to send to an external module which require it.
BB_SYSTEM_busy_Out	Output	1	0	Boolean signal to indicate if the module currently is busy or idle.
BB_SYSTEM_SCK_Out	Output	1	-	Slave Clock set to be a fraction lower than the system's clock; this fraction is defined in terms of a power 2 ratio.
BB_SYSTEM_data_Out	Output	8	00000000	Data bus signal with a byte size that carries the information coming from the slave.
BB_SYSTEM_CLOCK_50	Input	1	-	Clock of the system with a default value of 50MHz.
BB_SYSTEM_RESET_InHigh	Input	1	0	Reset signal in case of reload the initial values for the module.
BB_SYSTEM_MISO_In	Input	1	1	Receiver signal in charge of taking the data from the slave based on the clock ratio set.
BB_SYSTEM_start_InHigh	Input	1	0	Boolean signal to allow or not the module from an external signal.
BB_SYSTEM_data_In	Input	8	00000000	Data in terms of bytes to transmit.


2.1.4 Black box diagram

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies input/output signals for the product.

DELIVERABLES: Correct and complete diagram.

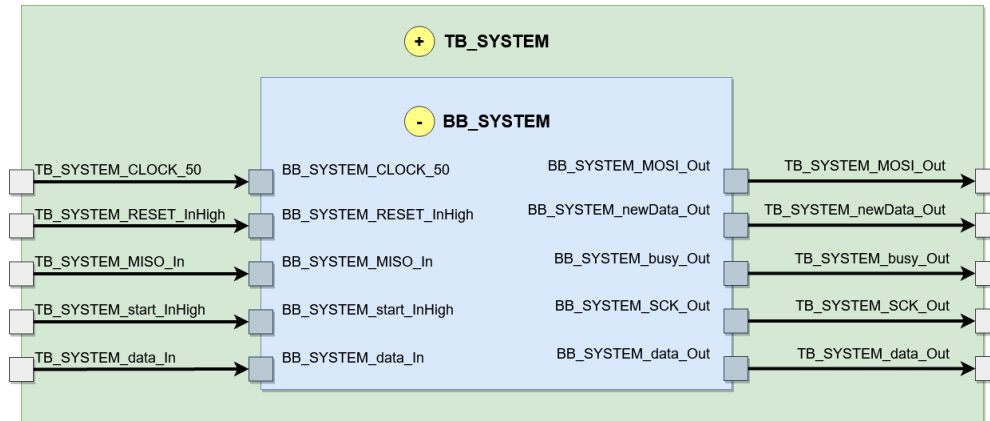- There is full correspondence between the black box diagram and the functionality of the requested component.
- The black box diagram shows all input and output signals with their corresponding structured names (In/Out) and sizes (bit/bus).
- The black box diagram relates that component to the characterization diagram (test-bench).



2.1.5 Functionality

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student breaks down the problem into a set of steps that respond to the expected functionality.

DELIVERABLES: Equation / Truth Table / Macro-algorithm correct and complete according to component functionality.

- The character equation and/or truth table and/or solution macro-algorithm correctly describes the functionality of the component and is properly represented by a detailed explanation where each step is less complex than the requested component.



Characteristic equation

$$data_Out[7:0] \leq (data_Out[7], data_Out[6], \dots, data_Out[0])_{CLOCK_RATIO} \leq MOSI_Out$$

$$(MISO_In)_{CLOCK_RATIO} \leq data_In[0]$$

$$(MISO_In)_{CLOCK_RATIO} \leq data_In[1]$$

...

$$(MISO_In)_{CLOCK_RATIO} \leq data_In[7]$$



Truth table

INPUTS			OUTPUTS		
RESET_In	MISO_In	start_In	MOSI_Out	newData_Out	busy_Out
1	1	0	1	0	0
1	1	1	1	0	0
0	1	0	1	0	0
0	1	1	1	0	1
0	0	1	0	0	1
0	0	1	1	0	1
0	1	1	0	0	1



Macro-algorithm

**Algorithm 4:** Master unit M**Data:**

RESET_In, MISO_In, start_In, [7:0] data_In

Algorithm:

MOSI_Out = 1

newData_Out = 0

busy_Out = 0

SCK_Out = 0000

data_Out = 00000000

counterBit = 0

CLOCK_RATIO = 4

if not RESET_In:

case state:

IDLE:

if start_In:

state = WAIT_HALF

WAIT_HALF:

SCK_Out += 1

if SCK_Out == (CLOCK_RATIO-1)[1]:

SCK_Out = 0000

state = TRANSFER

TRANSFER:

busy_Out = 1

SCK_Out += 1

if SCK_Out == (CLOCK_RATIO)[0]:

state = MOSI

else if SCK_Out == (CLOCK_RATIO-1)[1]:

state = READ_DATA

else if SCK_Out == (CLOCK_RATIO)[1]:

state = FULL

MOSI:

MOSI_Out = data_In[7]

SCK_Out += 1

state = TRANSFER

READ_DATA:

SCK_Out += 1

data_Out = [data_In[6:0], MISO_In]

state = TRANSFER

FULL:

busy_Out = 0

counterBit += 1

if counterBit == 7:

state = END

else:

state = TRANSFER

**Algorithm 5: Master unit M***END:**newData_Out = 1**counterBit = 0**state = IDLE**end case***Results:***MOSI_Out, newData_Out, busy_Out, SCK_Out[CLOCK_RATIO-1], [7:0] data_Out***2.1.6 Reference model****QUALITY PRODUCT:**

PEDAGOGICAL OBJECTIVE: The student proposes a reference model as function verification and control verification of RTL models, which can be constructed with software high level languages like C, C++, JavaScript, Python, etc.

DELIVERABLES: Source codes.

- The description in software language has similar structure to the hardware language algorithm.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.
- The validation model verifies the consistency of the RTL modules by judging whether the two designs are equivalent and consistent.

The source code below, just depicts the function based on the SPI Master White Box module. To consult the whole reference model, with the Black Box validation and the Simulation, it is necessary to visit the next online repository: https://github.com/favioacostad/SPI_IP_Core/tree/main/PJR0_SPI_MASTER/reference.

```

1  #=====
2  # LIBRARIES Definition
3  #=====
4  # Libraries required along the code
5  import numpy as np
6  np.set_printoptions(threshold = np.inf)
7  #from SPI_MASTER import *
8
9  #=====
10 # COMPLEMENTARY Function
11 #=====
12 # Function to emulate binary add operation in 8 size vector
13 def ADD_BIN (vector):
14     x = np.uint8(1)
15     # Vector is passed to decimal scalar
16     decV = np.array([vector[i]*2**(np.size(vector) - i - 1) for i in range(np.size(vector))])
17     add = sum(decV) + 1
18     # The reverse process is done and passed to binary vector
19     binV = np.array([1 if add & (1 << (np.size(vector) - j - 1)) else 0 for j in range(np.size(vector))], dtype = 'uint8')
20
21     return binV
22
23 #=====
24 # MODULE Definition
25 #=====
26 # Function describing SPI serial communication protocol for master devices
27 def SPI_MASTER (SPI_MASTER_CLOCK_50, SPI_MASTER_RESET_InHigh, SPI_MASTER_MISO_In, SPI_MASTER_start_InHigh,
28                 SPI_MASTER_data_In, CLOCK_RATIO, DATAWIDTH_BUS, STATE_SIZE):
29
30     #=====
31     # PARAMETER Declarations
32     #=====
33     #//////////////// STATES //////////////////
34     State_IDLE = np.uint8(0)
35     State_WAIT_HALF = np.uint8(1)
36     State_TRANSFER = np.uint8(2)
37     State_MOSI = np.uint8(3)
38     State_READ_DATA = np.uint8(4)
39     State_FULL = np.uint8(5)
40     State_END = np.uint8(6)
41     #//////////////// SIZES //////////////////
42
43     #=====
44     # PORT Declarations
45     #=====
46     #//////////////// OUTPUTS //////////////////
47     # Default values
48     SPI_MASTER_MOSI_Out = np.uint8(1)
49     SPI_MASTER_newData_Out = np.uint8(0)
50     SPI_MASTER_busy_Out = np.uint8(0)

```



```
51 SPI_MASTER_SCK_Out = np.uint8(0)
52 SPI_MASTER_data_Out = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')

54 #=====
55 # REG/WIRE Declarations
56 #=====
57 # Registers (Q)
58 global MOSI_Register, NewData_Register, Busy_Register, SCK_Register, DataOut_Register
59 global State_Register, MISO_Register, Start_Register, Data_Register, BitCounter_Register

61 #=====
62 # STRUCTURAL Coding
63 #=====
64 # INPUT LOGIC: Combinational
65 # Signals (D)
66 MISO_Signal = SPI_MASTER_MISO_In
67 Start_Signal = SPI_MASTER_start_InHigh
68 Data_Signal = Data_Register
69 BitCounter_Signal = BitCounter_Register

71 if State_Register == State_IDLE:
72     BitCounter_Signal = 0
73     if Start_Register:
74         State_Signal = State_WAIT_HALF
75     else:
76         State_Signal = State_IDLE

78 elif State_Register == State_WAIT_HALF:
79     Data_Signal = SPI_MASTER_data_In
80     if np.array_equal(SCK_Register[1:], np.ones(CLOCK_RATIO - 1, dtype = 'uint8')) and SCK_Register[0] == np.
        uint8(0):
81         State_Signal = State_TRANSFER
82     else:
83         State_Signal = State_WAIT_HALF

85 elif State_Register == State_TRANSFER:
86     if np.array_equal(SCK_Register, np.zeros(CLOCK_RATIO, dtype = 'uint8')):
87         State_Signal = State_MOSI
88     elif np.array_equal(SCK_Register[1:], np.ones(CLOCK_RATIO - 1, dtype = 'uint8')) and SCK_Register[0] == np.
        uint8(0):
89         State_Signal = State_READ_DATA
90     elif np.array_equal(SCK_Register, np.ones(CLOCK_RATIO, dtype = 'uint8')):
91         State_Signal = State_FULL
92     else:
93         State_Signal = State_TRANSFER

95 elif State_Register == State_MOSI:
96     State_Signal = State_TRANSFER

98 elif State_Register == State_READ_DATA:
99     State_Signal = State_TRANSFER
100     Data_Signal = np.array([Data_Register[k] for k in range(0,7)])
101     Data_Signal = np.insert(Data_Signal, 0, MISO_Register, axis = 0)

103 elif State_Register == State_FULL:
104     BitCounter_Signal = BitCounter_Register + 1;
105     if BitCounter_Register == DATAWIDTH_BUS-1:
106         State_Signal = State_END
107     else:
108         State_Signal = State_TRANSFER

110 elif State_Register == State_END:
111     State_Signal = State_IDLE
112     BitCounter_Signal = 0

114 else:
115     State_Signal = State_IDLE

117 #=====
118 # OUTPUTS
119 #=====
120 # OUTPUT LOGIC: Combinational
121 # Signals (D)
122 MOSI_Signal = MOSI_Register
123 NewData_Signal = NewData_Register
124 Busy_Signal = Busy_Register
125 SCK_Signal = SCK_Register
126 DataOut_Signal = DataOut_Register

128 if State_Register == State_IDLE:
129     MOSI_Signal = np.uint8(1)
130     NewData_Signal = np.uint8(0)
131     Busy_Signal = np.uint8(0)
132     SCK_Signal = np.zeros(CLOCK_RATIO, dtype = 'uint8')
133     DataOut_Signal = DataOut_Register

135 elif State_Register == State_WAIT_HALF:
136     MOSI_Signal = MOSI_Register
137     NewData_Signal = np.uint8(0)
138     Busy_Signal = np.uint8(0)
139     SCK_Signal = ADD_BIN(SCK_Register)
140     if np.array_equal(SCK_Register[1:], np.ones(CLOCK_RATIO - 1, dtype = 'uint8')) and SCK_Register[0] == np.
        uint8(0):
141         SCK_Signal = np.zeros(CLOCK_RATIO, dtype = 'uint8')
142     DataOut_Signal = DataOut_Register
```



```
144     elif State_Register == State_TRANSFER:
145         MOSI_Signal = MOSI_Register
146         NewData_Signal = np.uint8(0)
147         Busy_Signal = np.uint8(1)
148         SCK_Signal = ADD_BIN(SCK_Register)
149         DataOut_Signal = DataOut_Register
150
151     elif State_Register == State_MOSI:
152         MOSI_Signal = Data_Register[7]
153         NewData_Signal = np.uint8(0)
154         Busy_Signal = np.uint8(1)
155         SCK_Signal = ADD_BIN(SCK_Register)
156         DataOut_Signal = DataOut_Register
157
158     elif State_Register == State_READ_DATA:
159         MOSI_Signal = MOSI_Register
160         NewData_Signal = np.uint8(0)
161         Busy_Signal = np.uint8(1)
162         SCK_Signal = ADD_BIN(SCK_Register)
163         DataOut_Signal = DataOut_Register
164
165     elif State_Register == State_FULL:
166         MOSI_Signal = MOSI_Register
167         NewData_Signal = np.uint8(0)
168         Busy_Signal = np.uint8(0)
169         SCK_Signal = SCK_Register
170         DataOut_Signal = DataOut_Register
171
172     elif State_Register == State_END:
173         MOSI_Signal = MOSI_Register
174         NewData_Signal = np.uint8(1)
175         Busy_Signal = np.uint8(0)
176         SCK_Signal = SCK_Register
177         DataOut_Signal = Data_Register
178
179     else:
180         MOSI_Signal = np.uint8(1)
181         NewData_Signal = np.uint8(0)
182         Busy_Signal = np.uint8(0)
183         SCK_Signal = np.zeros(CLOCK_RATIO, dtype = 'uint8')
184         DataOut_Signal = DataOut_Register
185
186 # STATE REGISTER : Sequential
187 if SPI_MASTER_CLOCK_50:
188     # Updating global registers
189     if SPI_MASTER_RESET_InHigh:
190         MOSI_Register = np.uint8(1)
191         NewData_Register = np.uint8(0)
192         Busy_Register = np.uint8(0)
193         SCK_Register = np.zeros(CLOCK_RATIO, dtype = 'uint8')
194         DataOut_Register = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
195         State_Register = State_IDLE
196         MISO_Register = np.uint8(1)
197         Start_Register = np.uint8(0)
198         Data_Register = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
199         BitCounter_Register = 0
200     else:
201         MOSI_Register = MOSI_Signal
202         NewData_Register = NewData_Signal
203         Busy_Register = Busy_Signal
204         SCK_Register = SCK_Signal
205         DataOut_Register = DataOut_Signal
206         State_Register = State_Signal
207         MISO_Register = MISO_Signal
208         Start_Register = Start_Signal
209         Data_Register = Data_Signal
210         BitCounter_Register = BitCounter_Signal
211
212 # OUTPUT ASSIGNMENTS
213 SPI_MASTER_MOSI_Out = MOSI_Register
214 SPI_MASTER_newData_Out = NewData_Register
215 SPI_MASTER_busy_Out = Busy_Register
216 SPI_MASTER_SCK_Out = (int(not(not SCK_Register[0]) and ((State_Register == State_TRANSFER) or
217 (State_Register == State_MOSI) or
218 (State_Register == State_READ_DATA) or
219 (State_Register == State_FULL) or
220 (State_Register == State_END))))))
221
222 SPI_MASTER_data_Out = DataOut_Register
223
224 return SPI_MASTER_MOSI_Out, SPI_MASTER_newData_Out, SPI_MASTER_busy_Out, SPI_MASTER_SCK_Out, SPI_MASTER_data_Out
```

Archive 2.1: REF_SYSTEM.py



2.1.7 HDL: Black box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* #####
2  /** G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  #####
4  /** Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /** Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /**
7  /** This program is free software: you can redistribute it and/or modify
8  /** it under the terms of the GNU General Public License as published by
9  /** the Free Software Foundation, version 3 of the License.
10 /**
11 /** This program is distributed in the hope that it will be useful,
12 /** but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /** MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /** GNU General Public License for more details.
15 /**
16 /** You should have received a copy of the GNU General Public License
17 /** along with this program. If not, see <http://www.gnu.org/licenses/>
18 ##### */

20 //=====
21 // MODULE Definition
22 //=====
23 module BB_SYSTEM (
24 /////////////// OUTPUTS ///////////////////
25     BB_SYSTEM_MOSI_Out,
26     BB_SYSTEM_newData_Out,
27     BB_SYSTEM_busy_Out,
28     BB_SYSTEM_SCK_Out,
29     BB_SYSTEM_data_Out,
30 /////////////// INPUTS ///////////////////
31     BB_SYSTEM_CLOCK_50,
32     BB_SYSTEM_RESET_InHigh,
33     BB_SYSTEM_MISO_In,
34     BB_SYSTEM_start_InHigh,
35     BB_SYSTEM_data_In
36 );

38 //=====
39 // PARAMETER Declarations
40 //=====
41 // Data width of the input bus
42 parameter DATAWIDTH_BUS = 8;
43 // Size for the states needed into the protocol
44 parameter STATE_SIZE = 3;
45 // Value to specify how much be the clock for synchronizing Master and Slave
46 parameter CLOCK_RATIO = 4;

48 //=====
49 // PORT Declarations
50 //=====
51 /////////////// OUTPUTS ///////////////////
52 output BB_SYSTEM_MOSI_Out;
53 output BB_SYSTEM_newData_Out;
54 output BB_SYSTEM_busy_Out;
55 output BB_SYSTEM_SCK_Out;
56 output [DATAWIDTH_BUS-1:0] BB_SYSTEM_data_Out;
57 /////////////// INPUTS ///////////////////
58 input BB_SYSTEM_CLOCK_50;
59 input BB_SYSTEM_RESET_InHigh;
60 input BB_SYSTEM_MISO_In;
61 input BB_SYSTEM_start_InHigh;
62 input [DATAWIDTH_BUS-1:0] BB_SYSTEM_data_In;

64 //=====
65 // REG/WIRE Declarations
66 //=====

68 //=====
69 // STRUCTURAL Coding
70 //=====
71 SPI_MASTER #(CLOCK_RATIO(CLOCK_RATIO), .DATAWIDTH_BUS(DATAWIDTH_BUS), .STATE_SIZE(STATE_SIZE)) SPI_MASTER_u0 (
72 // Port map - connection between master ports and signals/registers
73 /////////////// OUTPUTS ///////////////////
74     .SPI_MASTER_MOSI_Out(BB_SYSTEM_MOSI_Out),
75     .SPI_MASTER_newData_Out(BB_SYSTEM_newData_Out),
76     .SPI_MASTER_busy_Out(BB_SYSTEM_busy_Out),
77     .SPI_MASTER_SCK_Out(BB_SYSTEM_SCK_Out),
78     .SPI_MASTER_data_Out(BB_SYSTEM_data_Out),
79 /////////////// INPUTS ///////////////////
80     .SPI_MASTER_CLOCK_50(BB_SYSTEM_CLOCK_50),

```



```

81 .SPI_MASTER_RESET_InHigh(BB_SYSTEM_RESET_InHigh) ,
82 .SPI_MASTER_MISO_In(BB_SYSTEM_MISO_In) ,
83 .SPI_MASTER_start_InHigh(BB_SYSTEM_start_InHigh) ,
84 .SPI_MASTER_data_In(BB_SYSTEM_data_In)
85 );
87 endmodule

```

Archive 2.2: BB_SYSTEM.v

2.1.8 Test vector definition

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student proposes a strategy to validate the functionality of the product.

DELIVERABLES: Clear selection strategies. Clear explanation of operation.

- Test vectors are selected by describing an explicit and clearly defined strategy in a paragraph, and these vectors allow you to fully verify functionality.

TEST VECTOR INPUTS			
RESET_In	MISO_In	start_In	data_In
1	1	0	00000000
0	1	0	00110000
0	1	1	00110000
0	0	1	00110000
0	1	1	00110000
0	1	1	00110000
0	0	1	00110000
0	1	1	00110000
0	0	1	00110000
0	1	1	00110000
0	0	1	00110000
0	1	0	00110000
0	1	0	00110001
0	1	1	00110001
0	...	1	...

The test vectors are composed first, by the reset input; second, by the MISO signal, responsible for the information coming from the slave; third, by the start input, which allows to start the module receiving information from an external module; and fourth, there's the eight bit size data input, that transport the information an external module requires to send. The subsequent values set to this data input are related with the ASCII (American Standard Code for Information Interchange) table and coincide to the characters: '0', '1', '2', '3', ..., '9'; 'a', 'b', 'c', ..., 'j'.

2.1.9 HDL: Test vectors

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1 /* *****
2 // # G0B1T: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3 // *****

```



```
4 4// Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5 5// Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6 6//
7 7// This program is free software: you can redistribute it and/or modify
8 8// it under the terms of the GNU General Public License as published by
9 9// the Free Software Foundation, version 3 of the License.
10 10//
11 11// This program is distributed in the hope that it will be useful,
12 12// but WITHOUT ANY WARRANTY; without even the implied warranty of
13 13// MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 14// GNU General Public License for more details.
15 15//
16 16// You should have received a copy of the GNU General Public License
17 17// along with this program. If not, see <http://www.gnu.org/licenses/>
18 18//***** */
19 19
20 20//=====
21 21// MODULE Definition
22 22//=====
23 23// Escala de tiempo
24 24`timescale 1 ns / 1 ns
25 25module TB_SYSTEM();
26 26// Constants
27 27//=====
28 28// Parameter (May differ for physical synthesis)
29 29//=====
30 30// General purpose registers
31 31reg eachvec;
32 32parameter TCK = 20; // Clock period in ns
33 33parameter CLK_FREQ = 1000000000 / TCK; // Frequency in HZ
34 34parameter DATAWIDTH_BUS = 8;
35 35parameter CLOCK_RATIO = 4; // CLOCK_RATIO = 1/16th (2^4 = 16 CLOCK cycles)
36 36
37 37// Test vector input registers
38 38
39 39//=====
40 40// INTERNAL WIRE/REG Declarations
41 41//=====
42 42// Wires (OUTPUTS)
43 43wire TB_SYSTEM_MOSI_Out;
44 44wire TB_SYSTEM_newData_Out;
45 45wire TB_SYSTEM_busy_Out;
46 46wire TB_SYSTEM_SCK_Out;
47 47wire [DATAWIDTH_BUS-1:0] TB_SYSTEM_data_Out;
48 48// Reg (INPUTS)
49 49reg TB_SYSTEM_CLOCK_50;
50 50reg TB_SYSTEM_RESET_InHigh;
51 51reg TB_SYSTEM_MISO_In;
52 52reg TB_SYSTEM_start_InHigh;
53 53reg [DATAWIDTH_BUS-1:0] TB_SYSTEM_data_In;
54 54
55 55// Assign statements (If any)
56 56BB_SYSTEM BB_SYSTEM_u0 (
57 57// Port map - connection between master ports and signals/registers
58 58//***** OUTPUTS *****/
59 59.BB_SYSTEM_MOSI_Out(TB_SYSTEM_MOSI_Out),
60 60.BB_SYSTEM_newData_Out(TB_SYSTEM_newData_Out),
61 61.BB_SYSTEM_busy_Out(TB_SYSTEM_busy_Out),
62 62.BB_SYSTEM_SCK_Out(TB_SYSTEM_SCK_Out),
63 63.BB_SYSTEM_data_Out(TB_SYSTEM_data_Out),
64 64//***** INPUTS *****/
65 65.BB_SYSTEM_CLOCK_50(TB_SYSTEM_CLOCK_50),
66 66.BB_SYSTEM_RESET_InHigh(TB_SYSTEM_RESET_InHigh),
67 67.BB_SYSTEM_MISO_In(TB_SYSTEM_MISO_In),
68 68.BB_SYSTEM_start_InHigh(TB_SYSTEM_start_InHigh),
69 69.BB_SYSTEM_data_In(TB_SYSTEM_data_In)
70 70);
71 71
72 72initial
73 73begin
74 74// Code that executes only once
75 75// Insert code here --> begin
76 76TB_SYSTEM_CLOCK_50 <= 0;
77 77// --> end
78 78$display("Running testbench");
79 79end
80 80
81 81always
82 82// Optional sensitivity list
83 83// @(Event1 or event2 or .... eventn)
84 84#(TCK/2) TB_SYSTEM_CLOCK_50 <= ~ TB_SYSTEM_CLOCK_50;
85 85
86 86initial begin
87 87// Code executes for every event on sensitivity list
88 88// Insert code here --> begin
89 89
90 90#0 TB_SYSTEM_RESET_InHigh <= 1'b1; TB_SYSTEM_MISO_In <= 1'b1; TB_SYSTEM_start_InHigh <= 1'b0;
91 91TB_SYSTEM_data_In <= 8'b00000000;
92 92
93 93#(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_MISO_In <= 1'b1; TB_SYSTEM_start_InHigh <= 1'b0;
94 94TB_SYSTEM_data_In <= 8'b00110000;
95 95
96 96#(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_MISO_In <= 1'b1; TB_SYSTEM_start_InHigh <= 1'b0;
97 97TB_SYSTEM_data_In <= 8'b00110000;
98 98
99 99#(64*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_MISO_In <= 1'b1; TB_SYSTEM_start_InHigh <= 1'b1;
100 100TB_SYSTEM_data_In <= 8'b00110000;
```



Archive 2.3: TB_SYSTEM.vt



2.1.10 White box diagram


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student makes a diagram of sub-components, signals and interconnections and makes a description of each sub-component.

DELIVERABLES: Diagram of sub-components, signals and interconnections, description of component or component to component.

- The white box diagram is correct and corresponds to the requested component.
- All internal and input/output signals with their corresponding structured names (In/Out) and sizes (Bit/Bus) are displayed for all internal system components.
- The white box diagram corresponds to an efficient solution in terms of resources, number of blocks and elements and solution algorithm. Internal components are less complex than those with higher hierarchy.
- A description (what is and how it works) of each of the constituent components of the requested component is presented, describing its signals.

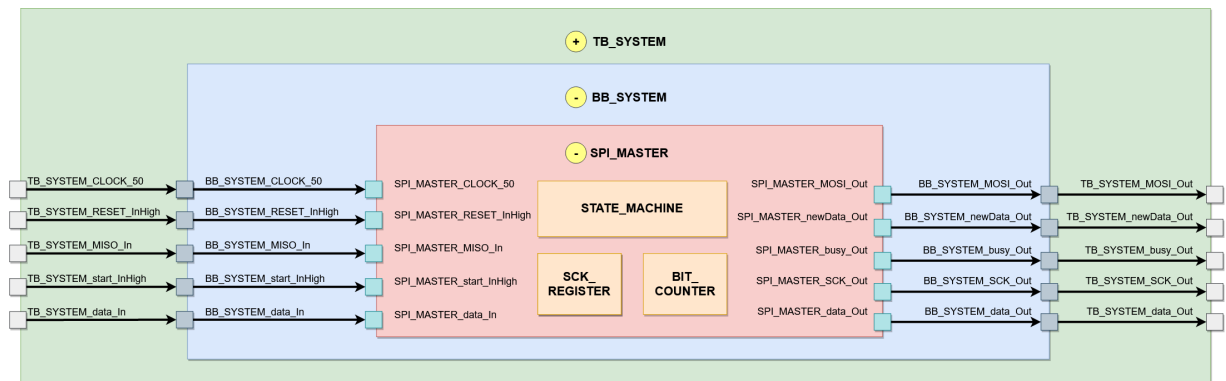For this specific case, the input/output ports match with the higher module into the hierarchical design.



2.1.11 HDL: White box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* =====
2  //  G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  // =====
4  //  Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  //  Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  //
7  //  This program is free software: you can redistribute it and/or modify
8  //  it under the terms of the GNU General Public License as published by
9  //  the Free Software Foundation, version 3 of the License.
10 //
11 //  This program is distributed in the hope that it will be useful,
12 //  but WITHOUT ANY WARRANTY; without even the implied warranty of
13 //  MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 //  GNU General Public License for more details.
15 //
16 //  You should have received a copy of the GNU General Public License
17 //  along with this program. If not, see <http://www.gnu.org/licenses/>
18 // ===== */
19
20 // =====
21 //  MODULE Definition
22 // =====
23 module SPI_MASTER #(parameter CLOCK_RATIO= 4, parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 // ===== OUTPUTS =====
25     SPI_MASTER_MOSI_Out,
26     SPI_MASTER_newData_Out,
27     SPI_MASTER_busy_Out,
28     SPI_MASTER_SCK_Out,
29     SPI_MASTER_data_Out,

```



```
30 //////////////// INPUTS ///////////////////
31 SPI_MASTER_CLOCK_50,
32 SPI_MASTER_RESET_InHigh,
33 SPI_MASTER_MISO_In,
34 SPI_MASTER_start_InHigh,
35 SPI_MASTER_data_In
36 );

37
38 //=====
39 // PARAMETER Declarations
40 //=====
41 //////////////// STATES ///////////////////
42 localparam State_IDLE = 3'b000;
43 localparam State_WAIT_HALF = 3'b001;
44 localparam State_TRANSFER = 3'b010;
45 localparam State_MOSI = 3'b011;
46 localparam State_READ_DATA = 3'b100;
47 localparam State_FULL = 3'b101;
48 localparam State_END = 3'b110;
49 //////////////// SIZES ///////////////////

50
51 //=====
52 // PORT Declarations
53 //=====
54 //////////////// OUTPUTS ///////////////////
55 output SPI_MASTER_MOSI_Out;
56 output SPI_MASTER_newData_Out;
57 output SPI_MASTER_busy_Out;
58 output SPI_MASTER_SCK_Out;
59 output [DATAWIDTH_BUS-1:0] SPI_MASTER_data_Out;
60 //////////////// INPUTS ///////////////////
61 input SPI_MASTER_CLOCK_50;
62 input SPI_MASTER_RESET_InHigh;
63 input SPI_MASTER_MISO_In;
64 input SPI_MASTER_start_InHigh;
65 input [DATAWIDTH_BUS-1:0] SPI_MASTER_data_In;
66 //////////////// FLAGS ///////////////////

67
68 //=====
69 // REG/WIRE Declarations
70 //=====
71 //////////////// REGISTERS ///////////////////
72 // Master Output Slave Input data transmitter
73 reg MOSI_Register;
74 // Boolean variable to inform of new data
75 reg NewData_Register;
76 // Boolean variable to indicate if the module is currently busy or idle
77 reg Busy_Register;
78 // Clock signal that synchronizes the Master and Slave modules
79 reg [CLOCK_RATIO-1:0] SCK_Register;
80 // Byte size register with the data to send to the master
81 reg [DATAWIDTH_BUS-1:0] DataOut_Register;
82 // Current state of the protocol
83 reg [STATE_SIZE-1:0] State_Register;
84 // Master Input Slave Output data transmitter
85 reg MISO_Register;
86 // Boolean variable to allow the module to start
87 reg Start_Register;
88 // Data in terms of bytes coming from the master
89 reg [DATAWIDTH_BUS-1:0] Data_Register;
90 // Counter for the number of bits carried out so far
91 reg [2:0] BitCounter_Register;
92 //////////////// SIGNALS ///////////////////
93 reg MOSI_Signal;
94 reg NewData_Signal;
95 reg Busy_Signal;
96 reg [CLOCK_RATIO-1:0] SCK_Signal;
97 reg [DATAWIDTH_BUS-1:0] DataOut_Signal;
98 reg [STATE_SIZE-1:0] State_Signal;
99 reg MISO_Signal;
100 reg Start_Signal;
101 reg [DATAWIDTH_BUS-1:0] Data_Signal;
102 reg [2:0] BitCounter_Signal;

103
104 //=====
105 // STRUCTURAL Coding
106 //=====
107 // INPUT LOGIC: Combinational
108 always @(*)
109 begin
110 // To init registers
111 MISO_Signal = SPI_MASTER_MISO_In;
112 Start_Signal = SPI_MASTER_start_InHigh;
113 Data_Signal = Data_Register;
114 BitCounter_Signal = BitCounter_Register;
115
116 case (State_Register)
117 State_IDLE:
118 begin
119 BitCounter_Signal = 3'b000;
120 if (Start_Register)
121 State_Signal = State_WAIT_HALF;
122 else
123 State_Signal = State_IDLE;
124 end
end
```



```
125 State_WAIT_HALF:
126     begin
127         Data_Signal = SPI_MASTER_data_In;
128         if (SCK_Register == {(CLOCK_RATIO-1){1'b1}})
129             State_Signal = State_TRANSFER;
130         else
131             State_Signal = State_WAIT_HALF;
132         end
133     end
134
135 State_TRANSFER:
136     begin
137         if (SCK_Register == {CLOCK_RATIO{1'b0}})
138             State_Signal = State_MOSI;
139         else if (SCK_Register == {(CLOCK_RATIO-1){1'b1}})
140             State_Signal = State_READ_DATA;
141         else if (SCK_Register == {CLOCK_RATIO{1'b1}})
142             State_Signal = State_FULL;
143         else
144             State_Signal = State_TRANSFER;
145         end
146     end
147
148 State_MOSI:
149     State_Signal = State_TRANSFER;
150
151 State_READ_DATA:
152     begin
153         State_Signal = State_TRANSFER;
154         Data_Signal = {Data_Register[6:0], MISO_Register};
155     end
156
157 State_FULL:
158     begin
159         BitCounter_Signal = BitCounter_Register + 1'b1;
160         if (BitCounter_Register == DATAWIDTH_BUS-1)
161             State_Signal = State_END;
162         else
163             State_Signal = State_TRANSFER;
164         end
165     end
166
167 State_END:
168     begin
169         State_Signal = State_IDLE;
170         BitCounter_Signal = 3'b000;
171     end
172
173 default: State_Signal = State_IDLE;
174 endcase
175 end
176
177 // STATE REGISTER : Sequential
178 always @(posedge SPI_MASTER_CLOCK_50, posedge SPI_MASTER_RESET_InHigh)
179     begin
180         if (SPI_MASTER_RESET_InHigh)
181             begin
182                 MOSI_Register <= 1'b1;
183                 NewData_Register <= 1'b0;
184                 Busy_Register <= 1'b0;
185                 SCK_Register <= {CLOCK_RATIO{1'b0}};
186                 DataOut_Register <= {DATAWIDTH_BUS{1'b0}};
187                 State_Register <= State_IDLE;
188                 MISO_Register <= 1'b1;
189                 Start_Register <= 1'b0;
190                 Data_Register <= {DATAWIDTH_BUS{1'b0}};
191                 BitCounter_Register <= 3'b000;
192             end
193         else
194             begin
195                 MOSI_Register <= MOSI_Signal;
196                 NewData_Register <= NewData_Signal;
197                 Busy_Register <= Busy_Signal;
198                 SCK_Register <= SCK_Signal;
199                 DataOut_Register <= DataOut_Signal;
200                 State_Register <= State_Signal;
201                 MISO_Register <= MISO_Signal;
202                 Start_Register <= Start_Signal;
203                 Data_Register <= Data_Signal;
204                 BitCounter_Register <= BitCounter_Signal;
205             end
206         end
207     end
208
209 // =====
210 // OUTPUTS
211 // =====
212 // OUTPUT LOGIC: Combinational
213 always @(*)
214     begin
215         // To init registers
216
217         case (State_Register)
218             State_IDLE:
219                 begin
220                     MOSI_Signal = 1'b1;
221                     NewData_Signal = 1'b0;
```



```
220     Busy_Signal = 1'b0;
221     SCK_Signal = {CLOCK_RATIO{1'b0}};
222     DataOut_Signal = DataOut_Register;
223 end
224
225 State_WAIT_HALF:
226 begin
227     MOSI_Signal = MOSI_Register;
228     NewData_Signal = 1'b0;
229     Busy_Signal = 1'b0;
230     SCK_Signal = SCK_Register + 1'b1;
231     if (SCK_Register == {(CLOCK_RATIO-1){1'b1}})
232         SCK_Signal = {CLOCK_RATIO{1'b0}};
233     DataOut_Signal = DataOut_Register;
234 end
235
236 State_TRANSFER:
237 begin
238     MOSI_Signal = MOSI_Register;
239     NewData_Signal = 1'b0;
240     Busy_Signal = 1'b1;
241     SCK_Signal = SCK_Register + 1'b1;
242     DataOut_Signal = DataOut_Register;
243 end
244
245 State_MOSI:
246 begin
247     MOSI_Signal = Data_Register[7];
248     NewData_Signal = 1'b0;
249     Busy_Signal = 1'b1;
250     SCK_Signal = SCK_Register + 1'b1;
251     DataOut_Signal = DataOut_Register;
252 end
253
254 State_READ_DATA:
255 begin
256     MOSI_Signal = MOSI_Register;
257     NewData_Signal = 1'b0;
258     Busy_Signal = 1'b1;
259     SCK_Signal = SCK_Register + 1'b1;
260     DataOut_Signal = DataOut_Register;
261 end
262
263 State_FULL:
264 begin
265     MOSI_Signal = MOSI_Register;
266     NewData_Signal = 1'b0;
267     Busy_Signal = 1'b0;
268     SCK_Signal = SCK_Register;
269     DataOut_Signal = DataOut_Register;
270 end
271
272 State_END:
273 begin
274     MOSI_Signal = MOSI_Register;
275     NewData_Signal = 1'b1;
276     Busy_Signal = 1'b0;
277     SCK_Signal = SCK_Register;
278     DataOut_Signal = Data_Register;
279 end
280
281 default:
282 begin
283     MOSI_Signal = 1'b1;
284     NewData_Signal = 1'b0;
285     Busy_Signal = 1'b0;
286     SCK_Signal = {CLOCK_RATIO{1'b0}};
287     DataOut_Signal = DataOut_Register;
288 end
289 endcase
290 end
291
292 // OUTPUT ASSIGNMENTS
293 assign SPI_MASTER_MOSI_Out = MOSI_Register;
294 assign SPI_MASTER_newData_Out = NewData_Register;
295 assign SPI_MASTER_busy_Out = Busy_Register;
296 assign SPI_MASTER_SCK_Out = ~(~SCK_Register[CLOCK_RATIO-1]) & ((State_Register == State_TRANSFER) | (
297     State_Register == State_MOSI) | (State_Register == State_READ_DATA) | (State_Register == State_FULL) | (
298     State_Register == State_END));
299 assign SPI_MASTER_data_Out = DataOut_Register;
300 endmodule
```

Archive 2.4: WB_SYSTEM.v



2.1.12 HDL: Blocks

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

From this particular case, there's no elements of lower hierarchy.

2.1.13 Temporal simulation


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates the functionality according to the proposed specifications with various types of tests.


DELIVERABLES: Functionality according to the proposed specifications and in various types of tests.

- Simulation results are presented for the requested product, explaining three or more operating cases on the simulation diagram. The simulation contains markers on the graph that indicate specific situations of the prototype.

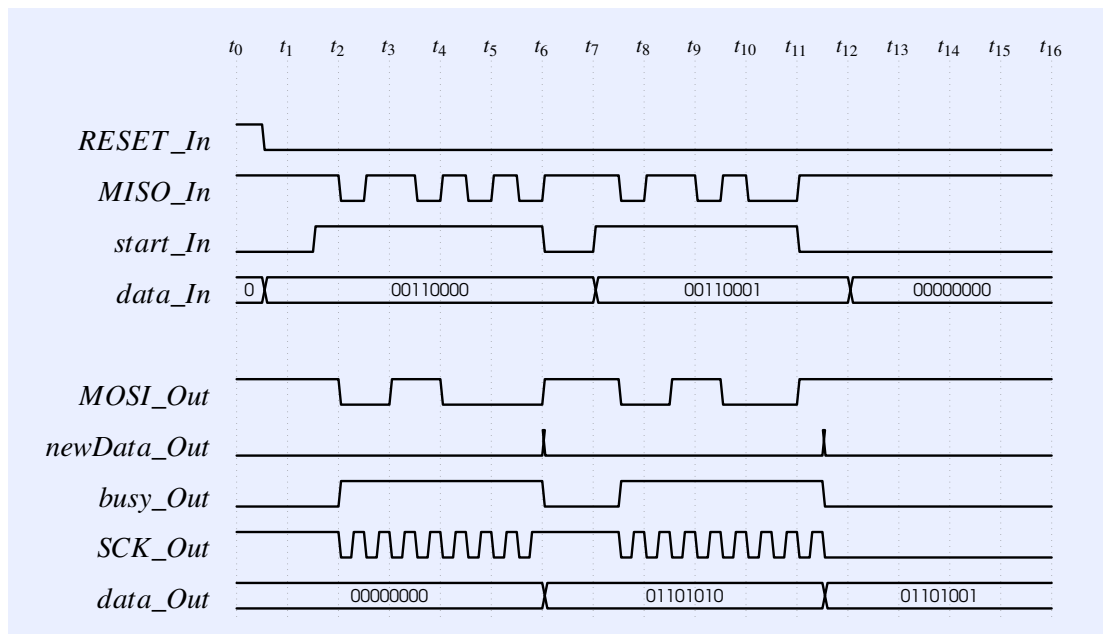Below is a diagram of what is expected to be obtained from the system. In this, despite the test vector layout includes an important quantity of bytes to transmit, the next diagram just cover a few data frames that exemplify the whole protocol procedure, which is the mayor purpose for this section.



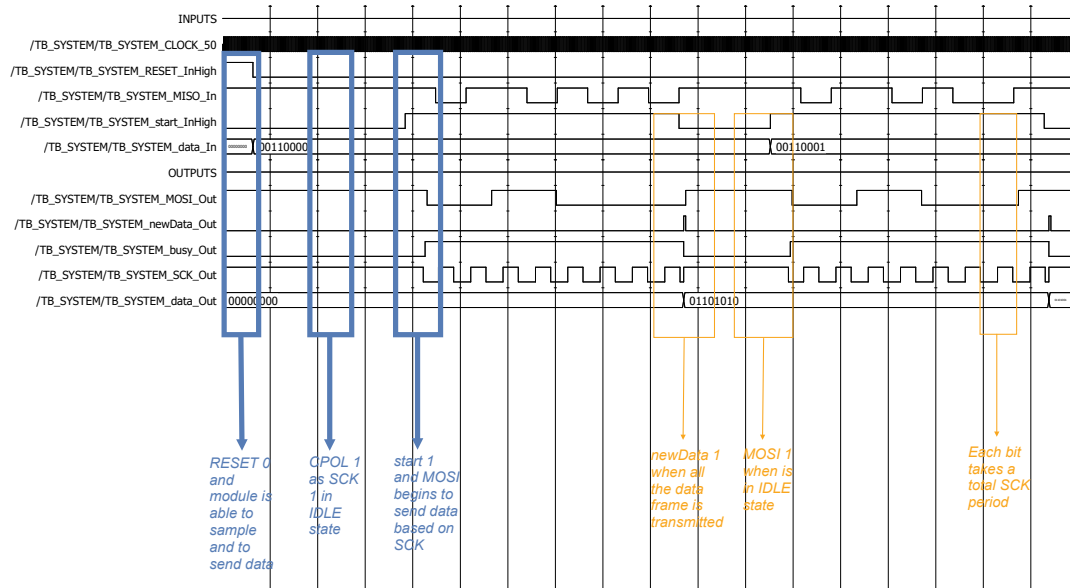On the other hand, the time diagram obtained in Altera's Quartus simulation tool is presented. In this case, we can check how it matches with what is expected. It is very important to highlight the sequential compound of this component, the 50MHz clock, which because of the very high frequency over the remaining signals, is depicted as a bold line.



2.1.14 Resource utilization

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student lists the resources used to build the module.

DELIVERABLES: A specific amount of resources in terms of quantity and percentage are presented.

- All the elements required for the module, as can be registers, logic gates and pins are enumerated. Besides, an explicit specification of the FPGA model used, is pointed out.

RESOURCE ELEMENT UTILIZATION		
Element	Amount	Percentage (Over total)
Logic gates	48	< 1%
Registers	35	-
Pins	24	16%
Device model	EP4CE22F17C6	
Family	Cyclone IV E	

2.1.15 Quartus diagrams

QUALITY PRODUCT:


PEDAGOGICAL OBJECTIVE: The student identifies elements of the Quartus Tool that can help the design process.

DELIVERABLES: Diagrams obtained in the tool.

- Diagrams obtained by Quartus are presented.




Block diagram

 



State machine diagram

 

2.1.16 Physical implementation

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student exposes a practical mode implementation to show the correct functionality of the core.

DELIVERABLES: Source codes and an abbreviated description of the way it was physically tested and the ports chosen as the I/O signals .

- The description is detailed at the point that can be recreated easily with the same features.
- All the source codes are included, even the ones detached to the HDL RTL codes.

To implement at physical level the Serial Peripheral Interface master, it was necessary to build another block shown below; this module is a counter, designed to increase by one as many times as a specific button is pressed. For this purpose, the total core had to be modified in terms of I/O signal ports and its connections between each other; the whole RTL source code can be consulted on the next online repository: https://github.com/favioacostad/SPI_IP_Core/tree/main/PJR0_SPI_MASTER/physical.

Additionally, the device which took the place of the slave peripheral, was an Arduino Nano board; thanks to its connection to a computer, it was possible to check into the Arduino IDE, the byte size values coming from the FPGA port assigned to MOSI. Correspondingly, a digital pin into the Arduino board was enable to be the MISO port and send data to an FPGA pin set as input; this configuration on the Arduino was possible thanks to the **SPI.h** library. Now, throughout an array of eight LED's, all the coming data bytes could be corroborated. Finally, the reset and start input signals, were allocated to a particular button as well.

```

1  /* *****
2  // G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  // *****
4  // Copyright (C) 2018, F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  // Copyright (C) 2020, F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  //
7  // This program is free software: you can redistribute it and/or modify
8  // it under the terms of the GNU General Public License as published by
9  // the Free Software Foundation, version 3 of the License.
10 //
11 // This program is distributed in the hope that it will be useful,
12 // but WITHOUT ANY WARRANTY; without even the implied warranty of
13 // MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 // GNU General Public License for more details.
15 //
16 // You should have received a copy of the GNU General Public License
17 // along with this program. If not, see <http://www.gnu.org/licenses/>
18 // ***** */
19
20 //=====
21 // MODULE Definition
22 //=====
23 module PULSE_COUNTER #(parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 /////////////// OUTPUTS ///////////////////
  
```



```
25 PULSE_COUNTER_start_Out ,
26 PULSE_COUNTER_data_Out ,
27 PULSE_COUNTER_dataCounter_Out ,
28 /////////////// INPUTS ///////////////
29 PULSE_COUNTER_CLOCK_50,
30 PULSE_COUNTER_RESET_InHigh,
31 PULSE_COUNTER_COUNT_InHigh,
32 PULSE_COUNTER_masterBusy_InHigh
33 );

34
35 //=====
36 // PARAMETER Declarations
37 //=====
38 /////////////// STATES ///////////////
39 localparam State_START = 3'b000;
40 localparam State_IDLE = 3'b001;
41 localparam State_LOAD = 3'b010;
42 localparam State_COUNT = 3'b011;
43
44 /////////////// SIZES ///////////////
45
46 //=====
47 // PORT Declarations
48 //=====
49 /////////////// OUTPUTS ///////////////
50 output PULSE_COUNTER_start_Out;
51 output [DATAWIDTH_BUS-1:0] PULSE_COUNTER_data_Out;
52 output [DATAWIDTH_BUS-1:0] PULSE_COUNTER_dataCounter_Out;
53 /////////////// INPUTS ///////////////
54 input PULSE_COUNTER_CLOCK_50;
55 input PULSE_COUNTER_RESET_InHigh;
56 input PULSE_COUNTER_COUNT_InHigh;
57 input PULSE_COUNTER_masterBusy_InHigh;
58 /////////////// FLAGS ///////////////
59
60 //=====
61 // REG/WIRE Declarations
62 //=====
63 /////////////// REGISTERS ///////////////
64 // Boolean variable to inform of new data
65 reg Start_Register;
66 // Data in terms of bytes
67 reg [DATAWIDTH_BUS-1:0] Data_Register;
68 // Current state of the protocol
69 reg [STATE_SIZE-1:0] State_Register;
70
71 /////////////// SIGNALS ///////////////
72 reg Start_Signal;
73 reg [DATAWIDTH_BUS-1:0] Data_Signal;
74 reg [STATE_SIZE-1:0] State_Signal;
75
76 //=====
77 // STRUCTURAL Coding
78 //=====
79 // INPUT LOGIC: Combinational
80 always @(*)
81 begin
82     case (State_Register)
83     State_START:
84         State_Signal = State_IDLE;
85
86     State_IDLE:
87         if (~PULSE_COUNTER_COUNT_InHigh)
88             State_Signal = State_LOAD;
89         else
90             State_Signal = State_IDLE;
91
92     State_LOAD:
93         if (PULSE_COUNTER_COUNT_InHigh)
94             State_Signal = State_COUNT;
95         else
96             State_Signal = State_LOAD;
97
98     State_COUNT:
99         if (~PULSE_COUNTER_COUNT_InHigh & ~PULSE_COUNTER_masterBusy_InHigh)
100             State_Signal = State_IDLE;
101         else
102             State_Signal = State_START;
103
104     default: State_Signal = State_START;
105     endcase
106 end
107
108 // STATE REGISTER : Sequential
109 always @(posedge PULSE_COUNTER_CLOCK_50, posedge PULSE_COUNTER_RESET_InHigh)
110 begin
111     if (PULSE_COUNTER_RESET_InHigh)
112     begin
113         Start_Register <= 1'b0;
114         Data_Register <= {DATAWIDTH_BUS{1'b0}};
115         State_Register <= State_START;
116     end
117
118     else
119     begin
```




```

120     Start_Register <= Start_Signal;
121     Data_Register <= Data_Signal;
122     State_Register <= State_Signal;
123 end
124 end

126 //=====
127 // OUTPUTS
128 //=====
129 // OUTPUT LOGIC: Combinational
130 always @(*)
131 begin
132     case (State_Register)
133     State_START:
134         begin
135             Start_Signal = 1'b0;
136             Data_Signal = Data_Register;
137         end
138
139     State_IDLE:
140         begin
141             Start_Signal = 1'b0;
142             Data_Signal = Data_Register;
143         end
144
145     State_LOAD:
146         begin
147             Start_Signal = 1'b0;
148             Data_Signal = Data_Register;
149         end
150
151     State_COUNT:
152         begin
153             Start_Signal = 1'b1;
154             Data_Signal = Data_Register + 8'b00000001;
155         end
156
157     default:
158         begin
159             Start_Signal = 1'b0;
160             Data_Signal = Data_Register;
161         end
162     endcase
163 end
164
165 // OUTPUT ASSIGNMENTS
167 assign PULSE_COUNTER_start_Out = Start_Register;
168 assign PULSE_COUNTER_data_Out = Data_Register;
169 assign PULSE_COUNTER_dataCounter_Out = Data_Register;
171 endmodule

```

Archive 2.5: PB_SYSTEM.v

2.1.17 Results and learnt lessons

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student discusses the design process identifying options for improvement and future work.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate and consistent).

- New specifications and applications of the work done (example: higher levels of complexity and uses in other contexts) are proposed.
- If the overall operating item is not achieved; identifies and argues the main reasons for non-functioning.
- Disciplinary language is accurate and appropriate, making use of grammatically correct phrases, without spelling errors.

The fact of Full Duplex transmission capacity, makes SPI standard a great protocol to implement in a particular scenery. Besides, its synchronicity allows to communicate with a peripheral at a frequency value as high as the device internal clock, taking into account though, the ceiling sequential limits the slave chips have.

It is necessary to mention the constraints this module has so far and the prospect IP core that can be implemented in the future. First, just one standard mode of operation was developed where **CPOL = 1** and **CPHA = 0**, which was chosen because it is the most applied into the practice; second, the layout proposed, just can accept one slave at a time; and third, the **SCK** clock signal for the slave, was determined to be as a quarter of the system's clock.



2.2 Slave (S)

Below, the serial communication component **SPI Slave (S)** is presented, showing its protocol to send and to receive information. To consult the whole SPI slave core and its source codes, the next repository link can be followed: https://github.com/favioacostad/SPI_IP_Core/tree/main/PJRO_SPI_SLAVE

2.2.1 Component description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student understands and proposes product specifications and restrictions.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate, and consistent) that explain: constraints, specifications, and search and identification of contexts where that component is used.

- The description of the component is written in the student words, organized logically and clearly.
- The specifications and restrictions fully respond to the requested component, demonstrating originality and own contributions.
- The search and identification of contexts where this component is used is clear.
- Discipline language is accurate and appropriate, phrases are grammatically correct and there are no spelling errors.

The Serial Peripheral Interface slave, is the complement of the master, exposed in the last section, and it works as well sequentially with the **SCK** clock input from the mentioned adept. Last signal frequency is usually designated by the available working range into the slave, which is in most of the cases the chip with lower capacity; moreover, this clock is commonly a fraction of the systems clock, named **CLOCK RATIO** for this particular case.

A mutual agreement, related to the protocol operation mode, has to be granted before starting to transmit data. In detail, the parameters **CPOL** and **CPHA** need to be with equal values for both sides. The mode designed in this application, is with **CPOL = 1** and **CPHA = 0**; nonetheless, it exists the possibility to adapt it for the remaining 3 modes. Last key point to cover are the voltage values that serve as the high and low logic levels; in the case of *DE0-Nano* where this component was developed, the values are **3.3V** and **0V** respectively.


2.2.2 Symbol

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates his component to a generic symbol usable in an architectural diagram.

DELIVERABLES: Correct and complete diagram.

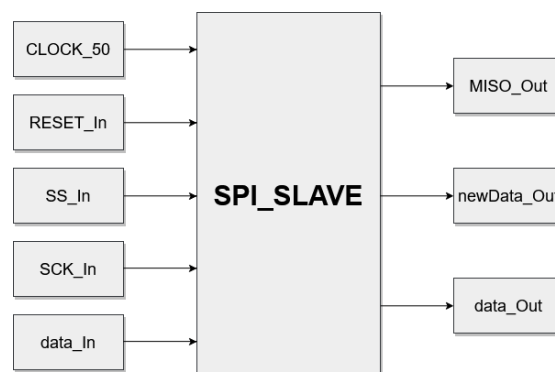- The symbol proposed to represent the component is based on symbols of a similar nature presented in the electronic component literature.





2.2.3 Port description

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student recognizes all the Input/Output (I/O) ports the module has.

DELIVERABLES: A description of each I/O port signal where its type, size and initial state are enunciated.

- The whole I/O signal ports are explicitly described and it is easy to understand the functionality for each one into the core.
- It is clear for the input ports, what kind of signal has to be stimulated to get a correct performance.

I/O Ports description				
Name	Signal type	Size	Initial state	Description
BB_SYSTEM_MISO_Out	Output	1	1	Transmitter signal designated to carry the data to the master based on the clock ratio set.
BB_SYSTEM_newData_Out	Output	1	0	Boolean variable to notify of new data ready to send to an external module which require it.
BB_SYSTEM_data_Out	Output	8	00000000	Data bus signal with 8 bit size that carries the information coming from the master.
BB_SYSTEM_CLOCK_50	Input	1	-	Clock of the system with a default value of 50MHz.
BB_SYSTEM_RESET_InHigh	Input	1	0	Reset signal in case of reload the initial values for the module.
BB_SYSTEM_SS_InLow	Input	1	1	Slave Select variable with the commission to activate or to deactivate the slave unit.
BB_SYSTEM_MOSI_In	Input	1	1	Receiver signal in charge of taking the data from the master based on the clock ratio set.
BB_SYSTEM_SCK_In	Input	1	-	Slave Clock set to be a fraction lower than the system's clock; this fraction is defined in terms of a power 2 ratio.
BB_SYSTEM_data_In	Input	8	00000000	Data in terms of bytes to transmit.


2.2.4 Black box diagram

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies input/output signals for the product.

DELIVERABLES: Correct and complete diagram.

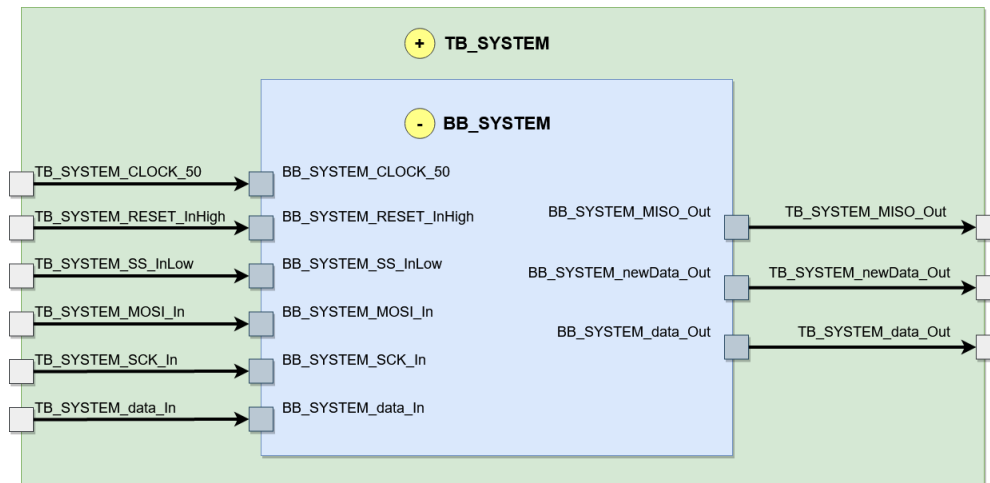- There is full correspondence between the black box diagram and the functionality of the requested component.
- The black box diagram shows all input and output signals with their corresponding structured names (In/Out) and sizes (bit/bus).
- The black box diagram relates that component to the characterization diagram (test-bench).



2.2.5 Functionality

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student breaks down the problem into a set of steps that respond to the expected functionality.

DELIVERABLES: Equation / Truth Table / Macro-algorithm correct and complete according to component functionality.

- The character equation and/or truth table and/or solution macro-algorithm correctly describes the functionality of the component and is properly represented by a detailed explanation where each step is less complex than the requested component.



Characteristic equation

$$(MOSI_In)_{CLOCK_RATIO} \leq data_In[0]$$

$$(MOSI_In)_{CLOCK_RATIO} \leq data_In[1]$$

...

$$(MOSI_In)_{CLOCK_RATIO} \leq data_In[7]$$

$$data_Out[7:0] \leq (data_Out[7], data_Out[6], ..., data_Out[0])_{CLOCK_RATIO} \leq MISO_Out$$



Truth table

INPUTS			OUTPUTS	
RESET_In	SS_In	MOSI_In	MISO_Out	newData_Out
1	1	1	1	0
1	0	1	1	0
0	1	1	1	0
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1



Macro-algorithm

**Algorithm 6:** Slave unit S**Data:**

RESET_In, SS_In, MOSI_In, SCK_In, [7:0] data_In

Algorithm:

MISO_Out = 1

newData_Out = 0

data_Out = 00000000

SCKOld = 0

counterBit = 0

CLOCK_RATIO = 4

if not RESET_In:

case state:

IDLE:

if SS_In:

MISO_Out = data_In[7]

else:

state = EDGE

EDGE:

if not SCKOld and SCK_In:

state = RISE_EDGE

else if SCKOld and not SCK_In:

state = FALL_EDGE

RISE_EDGE:

data_Out = [data_In[6:0], MOSI_In]

counterBit += 1

if counterBit == 7:

state = NEW_DATA

else:

state = EDGE

NEW_DATA:

counterBit = 0

state = EDGE

FALL_EDGE:

MISO_Out = data_In[7]

SCKOld = SCK_In

if SS_In:

state = IDLE

else:

state = EDGE

end case

Results:

MISO_Out, newData_Out, [7:0] data_Out



2.2.6 Reference model

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student proposes a reference model as function verification and control verification of RTL models, which can be constructed with software high level languages like C, C++, JavaScript, Python, etc.

DELIVERABLES: Source codes.

- The description in software language has similar structure to the hardware language algorithm.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.
- The validation model verifies the consistency of the RTL modules by judging whether the two designs are equivalent and consistent.

The source code below, just depicts the function based on the SPI Slave White Box module. To consult the whole reference model, with the Black Box validation and the Simulation, it is necessary to visit the next online repository: https://github.com/favioacostad/SPI_IP_Core/tree/main/PJR0_SPI_SLAVE/reference.

```

1  #=====
2  # LIBRARIES Definition
3  #=====
4  # Libraries required along the code
5  import numpy as np
6  np.set_printoptions(threshold = np.inf)
7  #from SPI_SLAVE import *
8
9  #=====
10 # COMPLEMENTARY Function
11 #=====
12 # Function to emulate binary add operation in 8 size vector
13 def ADD_BIN (vector):
14     x = np.uint8(1)
15     # Vector is passed to decimal scalar
16     decV = np.array([vector[i]*2**(np.size(vector) - i - 1) for i in range(np.size(vector))])
17     add = sum(decV) + 1
18     # The reverse process is done and passed to binary vector
19     binV = np.array([1 if add & (1 << (np.size(vector) - j - 1)) else 0 for j in range(np.size(vector))], dtype = 'uint8')
20
21     return binV
22
23 #=====
24 # MODULE Definition
25 #=====
26 # Function describing SPI serial communication protocol for slave peripherals
27 def SPI_SLAVE (SPI_SLAVE_CLOCK_50, SPI_SLAVE_RESET_InHigh, SPI_SLAVE_SS_InLow, SPI_SLAVE_MOSI_In,
28               SPI_SLAVE_SCK_In, SPI_SLAVE_data_In, DATAWIDTH_BUS, STATE_SIZE):
29
30     #=====
31     # PARAMETER Declarations
32     #=====
33     #//////// STATES //////////
34     State_IDLE = np.uint8(0)
35     State_EDGE = np.uint8(1)
36     State_RISE_EDGE = np.uint8(2)
37     State_NEW_DATA = np.uint8(3)
38     State_FALL_EDGE = np.uint8(4)
39     #//////// SIZES //////////
40
41     #=====
42     # PORT Declarations
43     #=====
44     #//////// OUTPUTS //////////
45     # Default values
46     SPI_SLAVE_MISO_Out = np.uint8(1)
47     SPI_SLAVE_newData_Out = np.uint8(0)
48     SPI_SLAVE_data_Out = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
49
50     #=====
51     # REG/WIRE Declarations
52     #=====
53     # Registers (Q)
54     global MISO_Register, NewData_Register, DataOut_Register, State_Register, SS_Register
55     global MOSI_Register, SCK_Register, SCKOld_Register, Data_Register, BitCounter_Register
56
57     #=====
58     # STRUCTURAL Coding
59     #=====
60     # INPUT LOGIC: Combinational
61     # Signals (D)
62     MOSI_Signal = SPI_SLAVE_MOSI_In
63     SS_Signal = SPI_SLAVE_SS_InLow
64     SCK_Signal = SPI_SLAVE_SCK_In
65     SCKOld_Signal = SCK_Register
66     Data_Signal = Data_Register
67     BitCounter_Signal = BitCounter_Register
68
69     if State_Register == State_IDLE:

```



```
70     if SS_Register:
71         State_Signal = State_IDLE
72         BitCounter_Signal = 0
73         Data_Signal = SPI_SLAVE_data_In
74     else:
75         State_Signal = State_EDGE
76
77     elif State_Register == State_EDGE:
78         if not SCKOld_Register and SCK_Register:
79             State_Signal = State_RISE_EDGE
80         elif SCKOld_Register and not SCK_Register:
81             State_Signal = State_FALL_EDGE
82         else:
83             State_Signal = State_EDGE
84
85     elif State_Register == State_RISE_EDGE:
86         BitCounter_Signal = BitCounter_Register + 1
87         Data_Signal = np.array([Data_Register[i] for i in range(0,7)])
88         Data_Signal = np.insert(Data_Signal,0,MOSI_Register,axis = 0)
89         if BitCounter_Register == DATAWIDTH_BUS-1:
90             State_Signal = State_NEW_DATA
91         else:
92             State_Signal = State_EDGE
93
94     elif State_Register == State_NEW_DATA:
95         State_Signal = State_EDGE
96         BitCounter_Signal = 0
97         Data_Signal = SPI_SLAVE_data_In
98
99     elif State_Register == State_FALL_EDGE:
100         if SS_Register:
101             State_Signal = State_IDLE
102         else:
103             State_Signal = State_EDGE
104
105     else:
106         State_Signal = State_IDLE
107
108     #=====
109     # OUTPUTS
110     #=====
111     # OUTPUT LOGIC: Combinational
112     # Signals (D)
113     MISO_Signal = MISO_Register
114     NewData_Signal = NewData_Register
115     DataOut_Register = DataOut_Register
116
117     if State_Register == State_IDLE:
118         MISO_Signal = Data_Register[7]
119         NewData_Signal = np.uint8(0)
120         DataOut_Signal = DataOut_Register
121
122     elif State_Register == State_EDGE:
123         MISO_Signal = MISO_Register
124         NewData_Signal = np.uint8(0)
125         DataOut_Signal = DataOut_Register
126
127     elif State_Register == State_RISE_EDGE:
128         MISO_Signal = MISO_Register
129         NewData_Signal = np.uint8(0)
130         DataOut_Signal = DataOut_Register
131
132     elif State_Register == State_NEW_DATA:
133         MISO_Signal = MISO_Register
134         NewData_Signal = np.uint8(1)
135         DataOut_Signal = Data_Register
136
137     elif State_Register == State_FALL_EDGE:
138         MISO_Signal = Data_Register[7]
139         NewData_Signal = np.uint8(0)
140         DataOut_Signal = DataOut_Register
141
142     else:
143         MISO_Signal = np.uint8(1)
144         NewData_Signal = np.uint8(0)
145         DataOut_Signal = DataOut_Register
146
147     # STATE REGISTER : Sequential
148     if SPI_SLAVE_CLOCK_50:
149         # Updating global registers
150         if SPI_SLAVE_RESET_InHigh:
151             MISO_Register = np.uint8(1)
152             NewData_Register = np.uint8(0)
153             DataOut_Register = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
154             State_Register = State_IDLE;
155             SS_Register = np.uint8(1)
156             MOSI_Register = np.uint8(1)
157             SCK_Register = np.uint8(0)
158             SCKOld_Register = np.uint8(0)
159             Data_Register = np.zeros(DATAWIDTH_BUS, dtype = 'uint8')
160             BitCounter_Register = 0
161         else:
162             MISO_Register = MISO_Signal
163             NewData_Register = NewData_Signal
164             DataOut_Register = DataOut_Signal
```



```

165         State_Register = State_Signal
166         SS_Register = SS_Signal
167         MOSI_Register = MOSI_Signal
168         SCK_Register = SCK_Signal
169         SCKOld_Register = SCKOld_Signal
170         Data_Register = Data_Signal
171         BitCounter_Register = BitCounter_Signal

173     # OUTPUT ASSIGNMENTS
174     SPI_SLAVE_MISO_Out = MISO_Register
175     SPI_SLAVE_newData_Out = NewData_Register
176     SPI_SLAVE_data_Out = DataOut_Register

178     return SPI_SLAVE_MISO_Out, SPI_SLAVE_newData_Out, SPI_SLAVE_data_Out

```

Archive 2.6: REF_SYSTEM.py

2.2.7 HDL: Black box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* *****
2  // # G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  // *****
4  // # Copyright (C) 2018. F.E. Segura Quijano (FES) fsegura@uniandes.edu.co
5  // # Copyright (C) 2020. F.A. Acosta David (FAD) fa.acostad@uniandes.edu.co
6  // #
7  // # This program is free software: you can redistribute it and/or modify
8  // # it under the terms of the GNU General Public License as published by
9  // # the Free Software Foundation, version 3 of the License.
10 // #
11 // # This program is distributed in the hope that it will be useful,
12 // # but WITHOUT ANY WARRANTY; without even the implied warranty of
13 // # MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 // # GNU General Public License for more details.
15 // #
16 // # You should have received a copy of the GNU General Public License
17 // # along with this program. If not, see <http://www.gnu.org/licenses/>
18 // ***** */

20 //=====
21 // MODULE Definition
22 //=====
23 module BB_SYSTEM (
24     /////////////// OUTPUTS ///////////////////
25     BB_SYSTEM_MISO_Out,
26     BB_SYSTEM_newData_Out,
27     BB_SYSTEM_data_Out,
28     /////////////// INPUTS ///////////////////
29     BB_SYSTEM_CLOCK_50,
30     BB_SYSTEM_RESET_InHigh,
31     BB_SYSTEM_SS_InLow,
32     BB_SYSTEM_MOSI_In,
33     BB_SYSTEM_SCK_In,
34     BB_SYSTEM_data_In
35 );

37 //=====
38 // PARAMETER Declarations
39 //=====
40 // Data width of the input bus
41 parameter DATAWIDTH_BUS = 8;
42 // Size for the states needed into the protocol
43 parameter STATE_SIZE = 3;

45 //=====
46 // PORT Declarations
47 //=====
48 /////////////// OUTPUTS ///////////////////
49 output BB_SYSTEM_MISO_Out;
50 output BB_SYSTEM_newData_Out;
51 output [DATAWIDTH_BUS-1:0] BB_SYSTEM_data_Out;
52 /////////////// INPUTS ///////////////////
53 input BB_SYSTEM_CLOCK_50;
54 input BB_SYSTEM_RESET_InHigh;
55 input BB_SYSTEM_SS_InLow;
56 input BB_SYSTEM_MOSI_In;
57 input BB_SYSTEM_SCK_In;
58 input [DATAWIDTH_BUS-1:0] BB_SYSTEM_data_In;

```




```

60 //=====
61 // REG/WIRE Declarations
62 //=====
63
64 //=====
65 // STRUCTURAL Coding
66 //=====
67 SPI_SLAVE #(.DATAWIDTH_BUS(DATAWIDTH_BUS), .STATE_SIZE(STATE_SIZE)) SPI_SLAVE_u0 (
68 // Port map – connection between master ports and signals/registers
69 /////////////// OUTPUTS ///////////////
70 .SPI_SLAVE_MISO_Out(BB_SYSTEM_MISO_Out),
71 .SPI_SLAVE_newData_Out(BB_SYSTEM_newData_Out),
72 .SPI_SLAVE_data_Out(BB_SYSTEM_data_Out),
73 /////////////// INPUTS ///////////////
74 .SPI_SLAVE_CLOCK_50(BB_SYSTEM_CLOCK_50),
75 .SPI_SLAVE_RESET_InHigh(BB_SYSTEM_RESET_InHigh),
76 .SPI_SLAVE_SS_InLow(BB_SYSTEM_SS_InLow),
77 .SPI_SLAVE_MOSI_In(BB_SYSTEM_MOSI_In),
78 .SPI_SLAVE_SCK_In(BB_SYSTEM_SCK_In),
79 .SPI_SLAVE_data_In(BB_SYSTEM_data_In)
80 );
82 endmodule

```

Archive 2.7: BB_SYSTEM.v

2.2.8 Test vector definition

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student proposes a strategy to validate the functionality of the product.

DELIVERABLES: Clear selection strategies. Clear explanation of operation.

- Test vectors are selected by describing an explicit and clearly defined strategy in a paragraph, and these vectors allow you to fully verify functionality.

TEST VECTOR INPUTS				
RESET_In	SS_In	MOSI_In	SCK_In	data_In
1	1	1	1	00000000
0	1	1	0	00000000
0	0	1	1	00110000
0	0	0	0	00110000
0	0	0	1	00110000
0	0	1	0	00110000
0	0	1	1	00110000
0	0	1	0	00110000
0	0	1	1	00110000
0	0	0	0	00110000
0	0	0	1	00110000
0	0	1	0	00110000
0	0	1	1	00110000
0	0	0	0	00110000
0	0	0	1	00110000
0	0	1	0	00110000
0	0	1	1	00110000
0	0	0	0	00110000
0	0	0	1	00110000
0	0	1	0	00110000
0	0	1	1	00110000
0	0	0	0	00110000
0	0	0	1	00110001
0	0	1	0	00110001
0	0	...	1	...

The test vectors are composed first, by the reset input; second, by the SS signal, with the aim to enable or not the slave module exchanging information with the master; third, by the MOSI input, with the mission to receive the eventual information from the opposite side; fourth, is the



SCK clock signal, which manage the rate to process the leaving and coming data; and fifth, the data input take place, in charge of the bytes an external module ask to transmit. The subsequent values are set to this data input which has the size of a byte (8 bits); these values are related with the ASCII (American Standard Code for Information Interchange) table and coincide to the characters: '0', '1', '2', '3', ..., '9'; 'a', 'b', 'c', ..., 'j'.

2.2.9 HDL: Test vectors

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* =====
2  // G0B1T: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  // =====
4  // Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  // Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  //
7  // This program is free software: you can redistribute it and/or modify
8  // it under the terms of the GNU General Public License as published by
9  // the Free Software Foundation, version 3 of the License.
10 //
11 // This program is distributed in the hope that it will be useful,
12 // but WITHOUT ANY WARRANTY; without even the implied warranty of
13 // MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 // GNU General Public License for more details.
15 //
16 // You should have received a copy of the GNU General Public License
17 // along with this program. If not, see <http://www.gnu.org/licenses/>
18 // ===== */
19
20 // =====
21 // MODULE Definition
22 // =====
23 // Escala de tiempo
24 `timescale 1 ns / 1 ns
25 module TB_SYSTEM();
26 // Constants
27 // =====
28 // Parameter (May differ for physical synthesis)
29 // =====
30 // General purpose registers
31 reg eachvec;
32 parameter TCK = 20; // Clock period in ns
33 parameter CLK_FREQ = 1000000000 / TCK; // Frequency in HZ
34 parameter DATAWIDTH_BUS = 8;
35 parameter CLOCK_RATIO = 4000; // CLOCK_RATIO = 1/16th (2^4 = 16 CLOCK cycles)
36
37 // Test vector input registers
38
39 // =====
40 // INTERNAL WIRE/REG Declarations
41 // =====
42 // Wires (OUTPUTS)
43 wire TB_SYSTEM_MISO_Out;
44 wire TB_SYSTEM_newData_Out;
45 wire [DATAWIDTH_BUS-1:0] TB_SYSTEM_data_Out;
46 // Reg (INPUTS)
47 reg TB_SYSTEM_CLOCK_50;
48 reg TB_SYSTEM_RESET_InHigh;
49 reg TB_SYSTEM_SS_InLow;
50 reg TB_SYSTEM_MOSI_In;
51 reg TB_SYSTEM_SCK_In;
52 reg [DATAWIDTH_BUS-1:0] TB_SYSTEM_data_In;
53
54 // Assign statements (If any)
55 BB_SYSTEM BB_SYSTEM_u0 (
56 // Port map - connection between master ports and signals/registers
57 // ===== OUTPUTS =====
58 .BB_SYSTEM_MISO_Out(TB_SYSTEM_MISO_Out),
59 .BB_SYSTEM_newData_Out(TB_SYSTEM_newData_Out),
60 .BB_SYSTEM_data_Out(TB_SYSTEM_data_Out),
61 // ===== INPUTS =====
62 .BB_SYSTEM_CLOCK_50(TB_SYSTEM_CLOCK_50),
63 .BB_SYSTEM_RESET_InHigh(TB_SYSTEM_RESET_InHigh),
64 .BB_SYSTEM_SS_InLow(TB_SYSTEM_SS_InLow),
65 .BB_SYSTEM_MOSI_In(TB_SYSTEM_MOSI_In),
66 .BB_SYSTEM_SCK_In(TB_SYSTEM_SCK_In),
67 .BB_SYSTEM_data_In(TB_SYSTEM_data_In)
68 );

```



```
69
70 initial
71 begin
72 // Code that executes only once
73 // Insert code here --> begin
74 TB_SYSTEM_CLOCK_50 <= 0;
75 TB_SYSTEM_SCK_In <= 1;
76 // --> end
77 $display("Running testbench");
78 end
79
80 always
81 // Optional sensitivity list
82 // @(Event1 or event2 or .... eventn)
83 #(TCK/2) TB_SYSTEM_CLOCK_50 <= ~ TB_SYSTEM_CLOCK_50;
84
85 always
86 #(16*(TCK/2)) TB_SYSTEM_SCK_In <= ~ TB_SYSTEM_SCK_In;
87
88 initial begin
89 // Code executes for every event on sensitivity list
90 // Insert code here --> begin
91
92 #0 TB_SYSTEM_RESET_InHigh <= 1'b1; TB_SYSTEM_SS_InLow <= 1'b1; TB_SYSTEM_MOSI_In <= 1'b1; TB_SYSTEM_data_In
    <= 8'b00000000;
93
94 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b1; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
95 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b1; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
96 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
97
98 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110000;
99 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
100 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
101 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110000;
102 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
103 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110000;
104 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110000;
105 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110000;
106
107 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110001;
108
109 #(16*8*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110001;
110 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110001;
111 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110001;
112 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110001;
113 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110001;
114 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110001;
115 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110001;
116 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110001;
117
118 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110010;
119
120 #(16*8*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110010;
121 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110010;
122 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110010;
123 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110010;
124 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b1;
    TB_SYSTEM_data_In <= 8'b00110010;
125 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110010;
126 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110010;
127 #(16*TCK) TB_SYSTEM_RESET_InHigh <= 1'b0; TB_SYSTEM_SS_InLow <= 1'b0; TB_SYSTEM_MOSI_In <= 1'b0;
    TB_SYSTEM_data_In <= 8'b00110010;
128
129 // #(TCK*10000) $finish;
130 @eachvec;
131 $finish;
132 // --> end
133 end
```



134 endmodule

Archive 2.8: TB_SYSTEM.vt

2.2.10 White box diagram


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student makes a diagram of sub-components, signals and interconnections and makes a description of each sub-component.

DELIVERABLES: Diagram of sub-components, signals and interconnections, description of component or component to component.

- The white box diagram is correct and corresponds to the requested component.
- All internal and input/output signals with their corresponding structured names (In/Out) and sizes (Bit/Bus) are displayed for all internal system components.
- The white box diagram corresponds to an efficient solution in terms of resources, number of blocks and elements and solution algorithm. Internal components are less complex than those with higher hierarchy.
- A description (what is and how it works) of each of the constituent components of the requested component is presented, describing its signals.

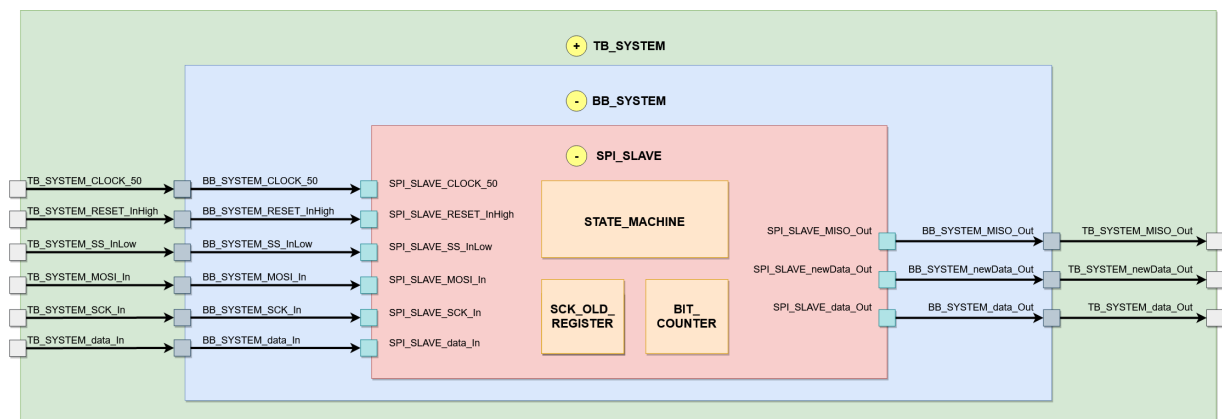For this specific case, the input/output ports match with the higher module into the hierarchical design.



2.2.11 HDL: White box

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

```

1  /* *****
2  /*  G0BIT: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  /* *****
4  /*  Copyright (C) 2018, F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  /*  Copyright (C) 2020, F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  /*
7  /*  This program is free software: you can redistribute it and/or modify
8  /*  it under the terms of the GNU General Public License as published by
9  /*  the Free Software Foundation, version 3 of the License.
10 /*
11 /*  This program is distributed in the hope that it will be useful,
12 /*  but WITHOUT ANY WARRANTY; without even the implied warranty of
13 /*  MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 /*  GNU General Public License for more details.
15 /*
16 /*  You should have received a copy of the GNU General Public License
17 /*  along with this program. If not, see <http://www.gnu.org/licenses/>
18 /* ***** */

```



```
20 //=====
21 // MODULE Definition
22 //=====
23 module SPI_SLAVE #(parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 /////////////// OUTPUTS ///////////////
25     SPI_SLAVE_MISO_Out,
26     SPI_SLAVE_newData_Out,
27     SPI_SLAVE_data_Out,
28 /////////////// INPUTS ///////////////
29     SPI_SLAVE_CLOCK_50,
30     SPI_SLAVE_RESET_InHigh,
31     SPI_SLAVE_SS_InLow,
32     SPI_SLAVE_MOSI_In,
33     SPI_SLAVE_SCK_In,
34     SPI_SLAVE_data_In
35 );
36
37 //=====
38 // PARAMETER Declarations
39 //=====
40 /////////////// STATES ///////////////
41 localparam State_IDLE = 3'b000;
42 localparam State_EDGE = 3'b001;
43 localparam State_RISE_EDGE = 3'b010;
44 localparam State_NEW_DATA = 3'b011;
45 localparam State_FALL_EDGE = 3'b100;
46 /////////////// SIZES ///////////////
47
48 //=====
49 // PORT Declarations
50 //=====
51 /////////////// OUTPUTS ///////////////
52 output SPI_SLAVE_MISO_Out;
53 output SPI_SLAVE_newData_Out;
54 output [DATAWIDTH_BUS-1:0] SPI_SLAVE_data_Out;
55 /////////////// INPUTS ///////////////
56 input SPI_SLAVE_CLOCK_50;
57 input SPI_SLAVE_RESET_InHigh;
58 input SPI_SLAVE_SS_InLow;
59 input SPI_SLAVE_MOSI_In;
60 input SPI_SLAVE_SCK_In;
61 input [DATAWIDTH_BUS-1:0] SPI_SLAVE_data_In;
62 /////////////// FLAGS ///////////////
63
64 //=====
65 // REG/WIRE Declarations
66 //=====
67 /////////////// REGISTERS ///////////////
68 // Master Input Slave Output data transmitter
69 reg MISO_Register;
70 // Boolean variable to inform of new data
71 reg NewData_Register;
72 // Byte size register with the data to send to the master
73 reg [DATAWIDTH_BUS-1:0] DataOut_Register;
74 // Current state of the protocol
75 reg [STATE_SIZE-1:0] State_Register;
76 // Shift Slave variable that points out if the master allows data transmission
77 reg SS_Register;
78 // Master Output Slave Input data transmitter
79 reg MOSI_Register;
80 // Clock signal that synchronizes the Master and Slave modules
81 reg SCK_Register;
82 // Value immediately prior to SCK signal
83 reg SCKOld_Register;
84 // Data in terms of bytes coming from the master
85 reg [DATAWIDTH_BUS-1:0] Data_Register;
86 // Counter for the number of bits carried out so far
87 reg [2:0] BitCounter_Register;
88 /////////////// SIGNALS ///////////////
89 reg MISO_Signal;
90 reg NewData_Signal;
91 reg [DATAWIDTH_BUS-1:0] DataOut_Signal;
92 reg [STATE_SIZE-1:0] State_Signal;
93 reg SS_Signal;
94 reg MOSI_Signal;
95 reg SCK_Signal;
96 reg SCKOld_Signal;
97 reg [DATAWIDTH_BUS-1:0] Data_Signal;
98 reg [2:0] BitCounter_Signal;
99
100 //=====
101 // STRUCTURAL Coding
102 //=====
103 // INPUT LOGIC: Combinational
104 always @(*)
105 begin
106     // To init registers
107     MOSI_Signal = SPI_SLAVE_MOSI_In;
108     SS_Signal = SPI_SLAVE_SS_InLow;
109     SCK_Signal = SPI_SLAVE_SCK_In;
110     SCKOld_Signal = SCK_Register;
111     Data_Signal = Data_Register;
112     BitCounter_Signal = BitCounter_Register;
113 end
```



```
114 case (State_Register)
115     State_IDLE:
116         begin
117             if (SS_Register)
118                 begin
119                     State_Signal = State_IDLE;
120                     BitCounter_Signal = 3'b000;
121                     Data_Signal = SPI_SLAVE_data_In;
122                 end
123             else
124                 State_Signal = State_EDGE;
125             end
126
127     State_EDGE:
128         begin
129             if (!SCKOld_Register && SCK_Register)
130                 State_Signal = State_RISE_EDGE;
131             else if (SCKOld_Register && !SCK_Register)
132                 State_Signal = State_FALL_EDGE;
133             else
134                 State_Signal = State_EDGE;
135             end
136
137     State_RISE_EDGE:
138         begin
139             BitCounter_Signal = BitCounter_Register + 1'b1;
140             Data_Signal = {Data_Register[6:0], MOSI_Register};
141             if (BitCounter_Register == DATAWIDTH_BUS-1)
142                 State_Signal = State_NEW_DATA;
143             else
144                 State_Signal = State_EDGE;
145             end
146
147     State_NEW_DATA:
148         begin
149             State_Signal = State_EDGE;
150             BitCounter_Signal = 3'b000;
151             Data_Signal = SPI_SLAVE_data_In;
152             end
153
154     State_FALL_EDGE:
155         begin
156             if (SS_Register)
157                 State_Signal = State_IDLE;
158             else
159                 State_Signal = State_EDGE;
160             end
161
162     default: State_Signal = State_IDLE;
163 endcase
164 end
165
166 // STATE REGISTER : Sequential
167 always @(posedge SPI_SLAVE_CLOCK_50, posedge SPI_SLAVE_RESET_InHigh)
168     begin
169         if (SPI_SLAVE_RESET_InHigh)
170             begin
171                 MISO_Register <= 1'b1;
172                 NewData_Register <= 1'b0;
173                 DataOut_Register <= {DATAWIDTH_BUS{1'b0}};
174                 State_Register <= State_IDLE;
175                 SS_Register <= 1'b1;
176                 MOSI_Register <= 1'b1;
177                 SCK_Register <= 1'b0;
178                 SCKOld_Register <= 1'b0;
179                 Data_Register <= {DATAWIDTH_BUS{1'b0}};
180                 BitCounter_Register <= 3'b000;
181             end
182
183         else
184             begin
185                 MISO_Register <= MISO_Signal;
186                 NewData_Register <= NewData_Signal;
187                 DataOut_Register <= DataOut_Signal;
188                 State_Register <= State_Signal;
189                 SS_Register <= SS_Signal;
190                 MOSI_Register <= MOSI_Signal;
191                 SCK_Register <= SCK_Signal;
192                 SCKOld_Register <= SCKOld_Signal;
193                 Data_Register <= Data_Signal;
194                 BitCounter_Register <= BitCounter_Signal;
195             end
196         end
197
198 //=====
199 // OUTPUTS
200 //=====
201 // OUTPUT LOGIC: Combinational
202 always @(*)
203     begin
204         // To init registers
205         // MISO_Signal = MISO_Register;
206         // NewData_Signal = NewData_Register;
207         // DataOut_Signal = DataOut_Register;
```



```
209 case (State_Register)
210   State_IDLE:
211     begin
212       MISO_Signal = Data_Register[7];
213       NewData_Signal = 1'b0;
214       DataOut_Signal = DataOut_Register;
215     end
216
217   State_EDGE:
218     begin
219       MISO_Signal = MISO_Register;
220       NewData_Signal = 1'b0;
221       DataOut_Signal = DataOut_Register;
222     end
223
224   State_RISE_EDGE:
225     begin
226       MISO_Signal = MISO_Register;
227       NewData_Signal = 1'b0;
228       DataOut_Signal = DataOut_Register;
229     end
230
231   State_NEW_DATA:
232     begin
233       MISO_Signal = MISO_Register;
234       NewData_Signal = 1'b1;
235       DataOut_Signal = Data_Register;
236     end
237
238   State_FALL_EDGE:
239     begin
240       MISO_Signal = Data_Register[7];
241       NewData_Signal = 1'b0;
242       DataOut_Signal = DataOut_Register;
243     end
244
245   default:
246     begin
247       MISO_Signal = 1'b1;
248       NewData_Signal = 1'b0;
249       DataOut_Signal = DataOut_Register;
250     end
251   endcase
252 end
253
254 // OUTPUT ASSIGNMENTS
255 assign SPI_SLAVE_MISO_Out = MISO_Register;
256 assign SPI_SLAVE_newData_Out = NewData_Register;
257 assign SPI_SLAVE_data_Out = DataOut_Register;
258
259 endmodule
```

Archive 2.9: WB_SYSTEM.v

2.2.12 HDL: Blocks

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies the basic elements of a project in the tool as well as the basic elements of the HDL language.

DELIVERABLES: Source codes.

- The description in hardware languages is correct and corresponds to the requested component.
- Complete documentation is included to structure and/or understand the code clearly (language indentation and syntax), correctly and appropriately naming all relevant signals, variables, and other elements.

From this particular case, there's no elements of lower hierarchy.

2.2.13 Temporal simulation

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student relates the functionality according to the proposed specifications with various types of tests.


DELIVERABLES: Functionality according to the proposed specifications and in various types of tests.

- Simulation results are presented for the requested product, explaining three or more operating cases on the simulation diagram. The simulation contains markers on the graph that indicate specific situations of the prototype.


Below is a diagram of what is expected to be obtained from the system. In this, despite the test vector layout includes an important quantity of bytes to transmit, the next diagram just cover



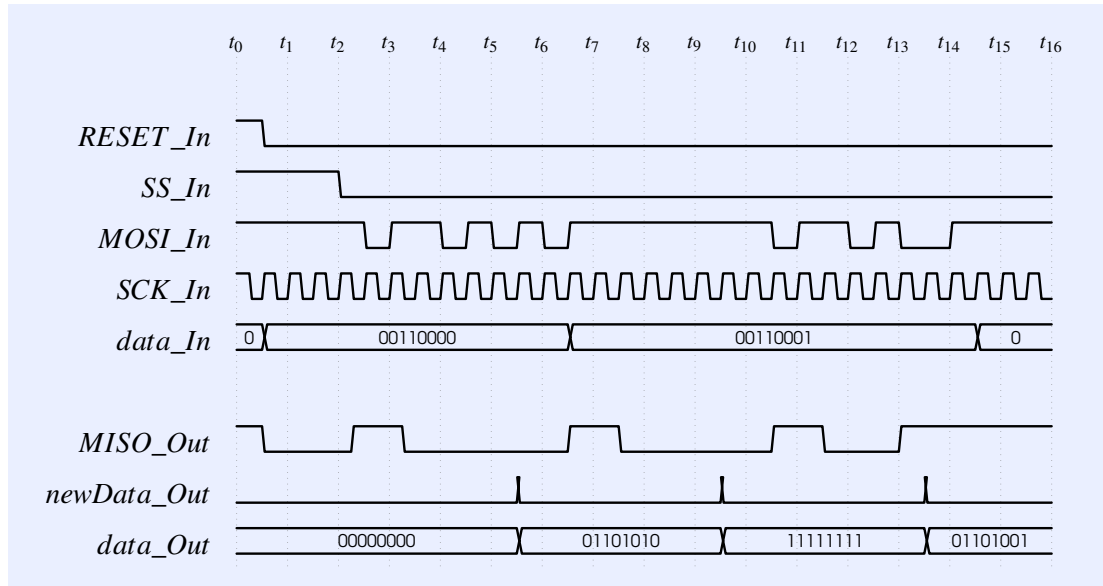a few data frames that exemplify the whole protocol procedure, which is the mayor purpose for this section.



On the other hand, the time diagram obtained in Altera's Quartus simulation tool is presented. In this case, we can check how it matches with what is expected, with only variations on MISO and MOSI ports due to the test performed for more bytes in this case. It is very important to highlight the sequential compound of this component, the 50MHz clock, which because of the very high frequency over the remaining signals, is depicted as a bold line.

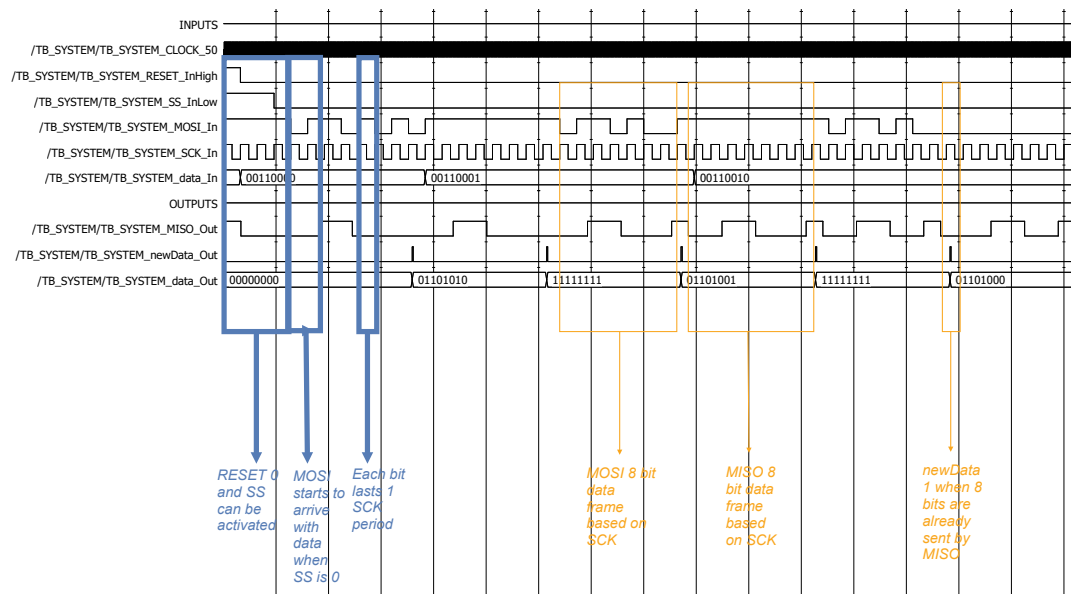

2.2.14 Resource utilization

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student lists the resources used to build the module.

DELIVERABLES: A specific amount of resources in terms of quantity and percentage are presented.

- All the elements required for the module, as can be registers, logic gates and pins are enumerated. Besides, an explicit specification of the FPGA model used, is pointed out.



RESOURCE ELEMENT UTILIZATION		
Element	Amount	Percentage (Over total)
Logic gates	32	< 1%
Registers	30	-
Pins	23	15%
Device model	EP4CE22F17C6	
Family	Cyclone IV E	

2.2.15 Quartus diagrams


QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student identifies elements of the Quartus Tool that can help the design process.


DELIVERABLES: Diagrams obtained in the tool.

- Diagrams obtained by Quartus are presented.

Block diagram

 

State machine diagram

 

2.2.16 Physical implementation

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student exposes a practical mode implementation to show the correct functionality of the core.

DELIVERABLES: Source codes and an abbreviated description of the way it was physically tested and the ports chosen as the I/O signals.

- The description is detailed at the point that can be recreated easily with the same features.
- All the source codes are included, even the ones detached to the HDL RTL codes.

To implement at physical level the Serial Peripheral Interface slave, it was necessary to build another block shown below; this module is a counter, designed to increase by one as many times



as a specific button is pressed. For this purpose, the total core had to be modified in terms of I/O signal ports and its connections between each other; the whole RTL source code can be consulted on the next online repository: https://github.com/favioacostad/SPI_IP_Core/tree/main/PJRO_SPI_SLAVE/physical.

Likewise, the device which took the place of the master module, was an Arduino Nano board; thanks to its connection to a computer, it was possible to check into the Arduino IDE, the byte size values coming from the FPGA port assigned to MISO. By the same token, a digital pin into the Arduino board was enable to be the MOSI port and send data to an FPGA pin, set as input, by following the SCK rate similarly interconnected; this configuration on the Arduino was possible thanks to the **SPI.h** library. Now, throughout an array of eight LED's, all the coming data bytes could be corroborated. Finally, the reset and SS enable input signals, were allocated to a particular button as well.

```
1  /s #####
2  // G0B1T: HDL SERIAL COMMUNICATION PROTOCOLS. 2020.
3  #####
4  // Copyright (C) 2018. F.E.Segura Quijano (FES) fsegura@uniandes.edu.co
5  // Copyright (C) 2020. F.A.Acosta David (FAD) fa.acostad@uniandes.edu.co
6  //
7  // This program is free software: you can redistribute it and/or modify
8  // it under the terms of the GNU General Public License as published by
9  // the Free Software Foundation, version 3 of the License.
10 //
11 // This program is distributed in the hope that it will be useful,
12 // but WITHOUT ANY WARRANTY; without even the implied warranty of
13 // MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
14 // GNU General Public License for more details.
15 //
16 // You should have received a copy of the GNU General Public License
17 // along with this program. If not, see <http://www.gnu.org/licenses/>
18 ##### s/

20 //=====
21 // MODULE Definition
22 //=====
23 module PULSE_COUNTER #(parameter DATAWIDTH_BUS = 8, parameter STATE_SIZE = 3)(
24 /////////////// OUTPUTS ///////////////////
25     PULSE_COUNTER_data_Out,
26     PULSE_COUNTER_dataCounter_Out,
27 /////////////// INPUTS ///////////////////
28     PULSE_COUNTER_CLOCK_50,
29     PULSE_COUNTER_RESET_InHigh,
30     PULSE_COUNTER_COUNT_InHigh,
31     PULSE_COUNTER_SS_InLow,
32     PULSE_COUNTER_slaveNewData_InHigh
33 );

35 //=====
36 // PARAMETER Declarations
37 //=====
38 /////////////// STATES ///////////////////
39 localparam State_ENABLE = 3'b000;
40 localparam State_IDLE = 3'b001;
41 localparam State_LOAD = 3'b010;
42 localparam State_COUNT = 3'b011;

44 /////////////// SIZES ///////////////////

46 //=====
47 // PORT Declarations
48 //=====
49 /////////////// OUTPUTS ///////////////////
50 output [DATAWIDTH_BUS-1:0] PULSE_COUNTER_data_Out;
51 output [DATAWIDTH_BUS-1:0] PULSE_COUNTER_dataCounter_Out;
52 /////////////// INPUTS ///////////////////
53 input PULSE_COUNTER_CLOCK_50;
54 input PULSE_COUNTER_RESET_InHigh;
55 input PULSE_COUNTER_COUNT_InHigh;
56 input PULSE_COUNTER_SS_InLow;
57 input PULSE_COUNTER_slaveNewData_InHigh;
58 /////////////// FLAGS ///////////////////

60 //=====
61 // REG/WIRE Declarations
62 //=====
63 /////////////// REGISTERS ///////////////////
64 // Boolean variable to inform new data can be sent
65 reg Enable_Register;
66 // Data in terms of bytes
67 reg [DATAWIDTH_BUS-1:0] Data_Register;
68 // Current state of the protocol
69 reg [STATE_SIZE-1:0] State_Register;
```



```
71 ////////////// SIGNALS //////////////////
72 reg Enable_Signal;
73 reg [DATAWIDTH_BUS-1:0] Data_Signal;
74 reg [STATE_SIZE-1:0] State_Signal;

75 //=====
76 // STRUCTURAL Coding
77 //=====
78 // INPUT LOGIC: Combinational
79 always @(*)
80 begin
81     // To init registers
82     Enable_Signal = PULSE_COUNTER_SS_InLow;
83
84     case (State_Register)
85     State_ENABLE:
86         if (Enable_Register)
87             State_Signal = State_ENABLE;
88         else
89             State_Signal = State_IDLE;
90
91     State_IDLE:
92         if (~PULSE_COUNTER_COUNT_InHigh)
93             State_Signal = State_LOAD;
94         else
95             State_Signal = State_IDLE;
96
97     State_LOAD:
98         if (PULSE_COUNTER_COUNT_InHigh)
99             State_Signal = State_COUNT;
100        else
101            State_Signal = State_LOAD;
102
103     State_COUNT:
104         if (~PULSE_COUNTER_COUNT_InHigh && PULSE_COUNTER_slaveNewData_InHigh)
105             State_Signal = State_IDLE;
106         else
107             State_Signal = State_ENABLE;
108
109     default: State_Signal = State_ENABLE;
110 endcase
111 end
112
113 // STATE REGISTER : Sequential
114 always @(posedge PULSE_COUNTER_CLOCK_50, posedge PULSE_COUNTER_RESET_InHigh)
115 begin
116     if (PULSE_COUNTER_RESET_InHigh)
117     begin
118         Enable_Register <= 1'b1;
119         Data_Register <= {DATAWIDTH_BUS{1'b0}};
120         State_Register <= State_ENABLE;
121     end
122
123     else
124     begin
125         Enable_Register <= Enable_Signal;
126         Data_Register <= Data_Signal;
127         State_Register <= State_Signal;
128     end
129 end
130
131 //=====
132 // OUTPUTS
133 //=====
134 // OUTPUT LOGIC: Combinational
135 always @(*)
136 begin
137     case (State_Register)
138     State_ENABLE:
139         Data_Signal = Data_Register;
140
141     State_IDLE:
142         Data_Signal = Data_Register;
143
144     State_LOAD:
145         Data_Signal = Data_Register;
146
147     State_COUNT:
148         Data_Signal = Data_Register + 8'b00000001;
149
150     default: Data_Signal = Data_Register;
151 endcase
152 end
153
154 // OUTPUT ASSIGNMENTS
155 assign PULSE_COUNTER_data_Out = Data_Register;
156 assign PULSE_COUNTER_dataCounter_Out = Data_Register;
157
158 endmodule
```

Archive 2.10: PB_SYSTEM.v



2.2.17 Results and learnt lessons

QUALITY PRODUCT:

PEDAGOGICAL OBJECTIVE: The student discusses the design process identifying options for improvement and future work.

DELIVERABLES: Contains a maximum of two paragraphs (clear, accurate and consistent).

- a. New specifications and applications of the work done (example: higher levels of complexity and uses in other contexts) are proposed.
- b. If the overall operating item is not achieved; identifies and argues the main reasons for non-functioning.
- c. Disciplinary language is accurate and appropriate, making use of grammatically correct phrases, without spelling errors.

To deal with the SPI communication protocol, there's no need to check the data frame format, because the standard itself only allows the 8 data bits without start/end bits or parity error detection bits; this can be an advantage, regarding the compatibility among chips. Even though, SPI depends on the **CPOL** and **CPHA** operation modes which are related with the SCK clock signal, and on the contrary, can diminish the compatibility mentioned.

In the light of adopting a multi slave architecture, first is necessary to set up a configuration with multiple SS signals wired to each slave or, on the other hand, one SS signal connected through a Daisy chain mechanism. Last implementations suggest a minimum amount of changes to the core already developed.